



Chipsmall Limited consists of a professional team with an average of over 10 year of expertise in the distribution of electronic components. Based in Hongkong, we have already established firm and mutual-benefit business relationships with customers from,Europe,America and south Asia,supplying obsolete and hard-to-find components to meet their specific needs.

With the principle of “Quality Parts,Customers Priority,Honest Operation,and Considerate Service”,our business mainly focus on the distribution of electronic components. Line cards we deal with include Microchip,ALPS,ROHM,Xilinx,Pulse,ON,Everlight and Freescale. Main products comprise IC,Modules,Potentiometer,IC Socket,Relay,Connector.Our parts cover such applications as commercial,industrial, and automotives areas.

We are looking forward to setting up business relationship with you and hope to provide you with the best service and solution. Let us make a better world for our industry!



Contact us

Tel: +86-755-8981 8866 Fax: +86-755-8427 6832

Email & Skype: info@chipsmall.com Web: www.chipsmall.com

Address: A1208, Overseas Decoration Building, #122 Zhenhua RD., Futian, Shenzhen, China







ESSENTIAL INFORMATION

BUILD INSTRUCTIONS
CHECKING YOUR PCB & FAULT-FINDING
MECHANICAL DETAILS
HOW THE KIT WORKS

INVESTIGATE THE 555 TIMER CHIP WITH THIS

555 TIMER ASTABLE KIT

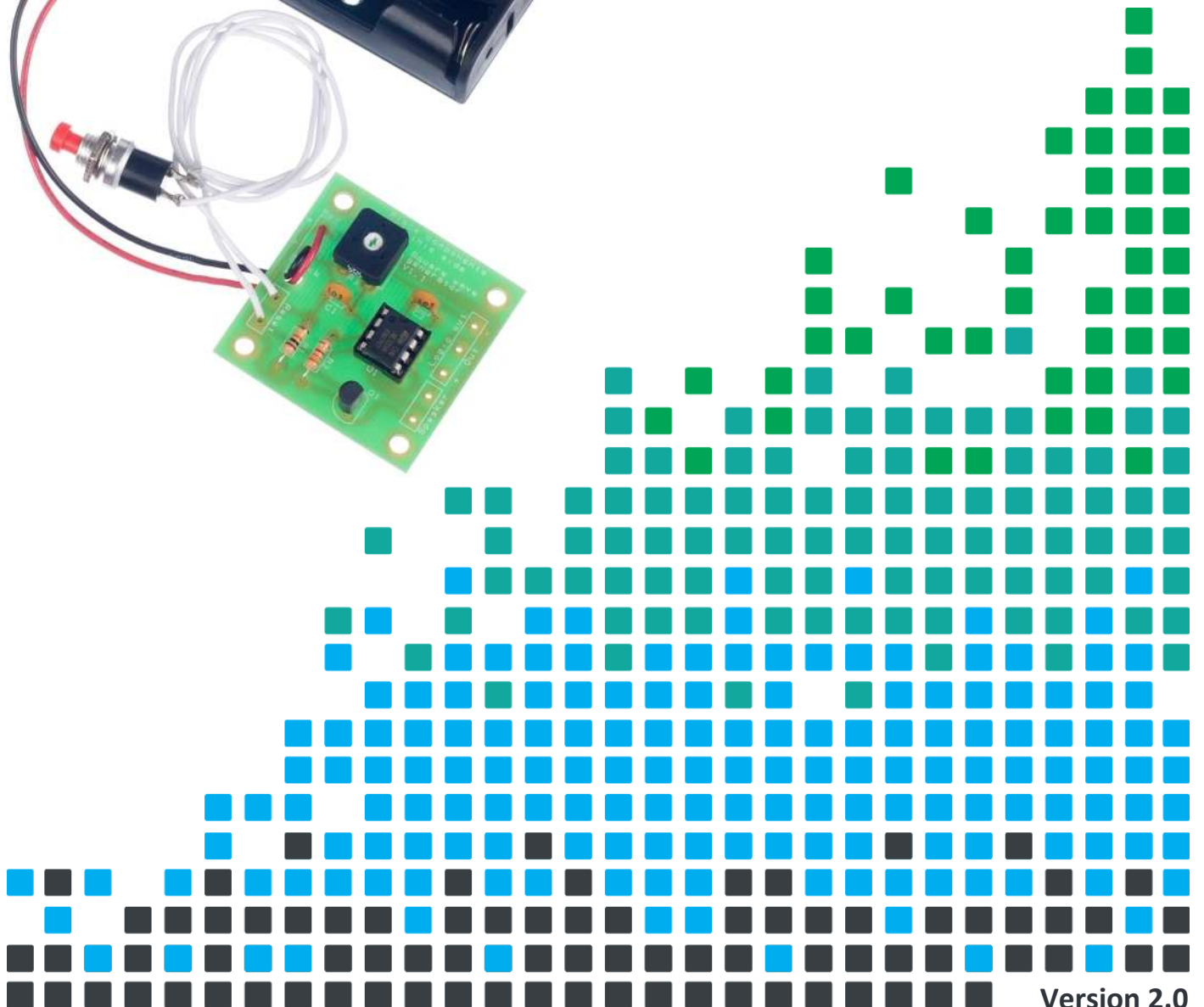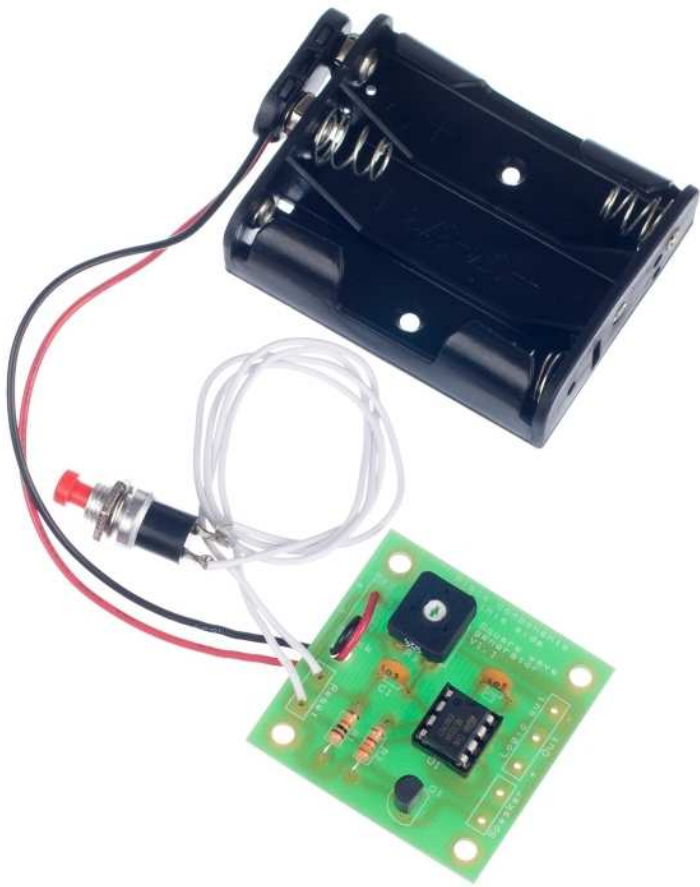

Version 2.0

Build Instructions

Before you start, take a look at the Printed Circuit Board (PCB). The components go in the side with the writing on and the solder goes on the side with the tracks and silver pads.

1 PLACE RESISTORS

Start with the two resistors:
The text on the PCB shows where R1, R2 etc go.
Ensure that you put the resistors in the right place.

PCB Ref	Value	Colour Bands
R1	10K Ω	Brown, black, orange
R2	3.3K Ω	Orange, orange, red



2 SOLDER THE CAPACITORS

Place the two 10nF capacitors into the board where it is labelled C1 and C2. It does not matter which way around the devices are fitted.



3 SOLDER THE TRANSISTOR

Place the BC547 transistor into the board where it is labelled Q1. Make sure that the device is the correct way around. The shape of the device should match the outline on the PCB.



4 SOLDER THE POTENTIOMETER

The 47K Ω variable potentiometers should be soldered into R3 on the PCB. The legs on the device should be matched with the holes on the PCB.



5 SOLDER THE IC HOLDER


Solder the Integrated Circuit (IC) holder into U1. When putting it into the board, be sure to get it the right way around. The notch on the IC holder should line up with the notch on the lines marked on the PCB.



6 ATTACH THE BATTERY CLIP

Now you must attach the battery clip. Start by feeding the leads through the strain relief hole between the power and reset connections. The wire should be fed in from the rear of the board (see right, below).

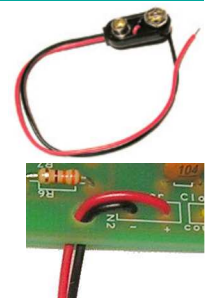The leads should be connected to the 'Power' terminals. The red lead should be soldered to the '+' terminal (also marked with text 'red') and the black lead should be soldered to the '-' terminal (also marked with the text 'black').



555 Timer Astable Essentials

www.kitronik.co.uk/2117



7

CONNECT THE SPEAKER

To connect the speaker to you need to cut two pieces of wire to the desired length. Strip both ends and solder them into 'Speaker' and the other end to the tabs on the speaker. The wires can go either way around.



8

SOLDER THE SWITCH

Cut and strip two pieces of wire to the required length for connecting to the switch. Solder one end of each wire to each of the terminals on the switch and the other end to the terminals labelled 'Reset'. It does not matter which wire goes to which terminal.



9

INSERT THE IC INTO HOLDER

The IC can now be put into the holder, ensuring that the notch on the chip lines up with the notch on the holder.



Using the Logic Output

The square wave generator board can be used to drive logic instead of a speaker. When the logic output is to be used the speaker doesn't need to be present and connections to the 'logic out' can be made as follows:

- + This is the positive power
- This is 0 Volts
- Out This is the logic level output

Checking Your PCB

Check the following before you power up the unit:

Check the bottom of the board to ensure that:


- All holes (except the large mounting holes) are filled with the lead of a component.
- All these leads are soldered.
- Pins next to each other are not soldered together.

Check the top of the board to ensure that:


- The notch on the 555 IC matches the outline on the PCB.
- The shape of the transistor matches the outline on the PCB.
- The resistor bands on R1 are brown, black and orange.
- All the connecting leads are connected to the right part and that the power connection is the right way around.



Fault finding flow chart

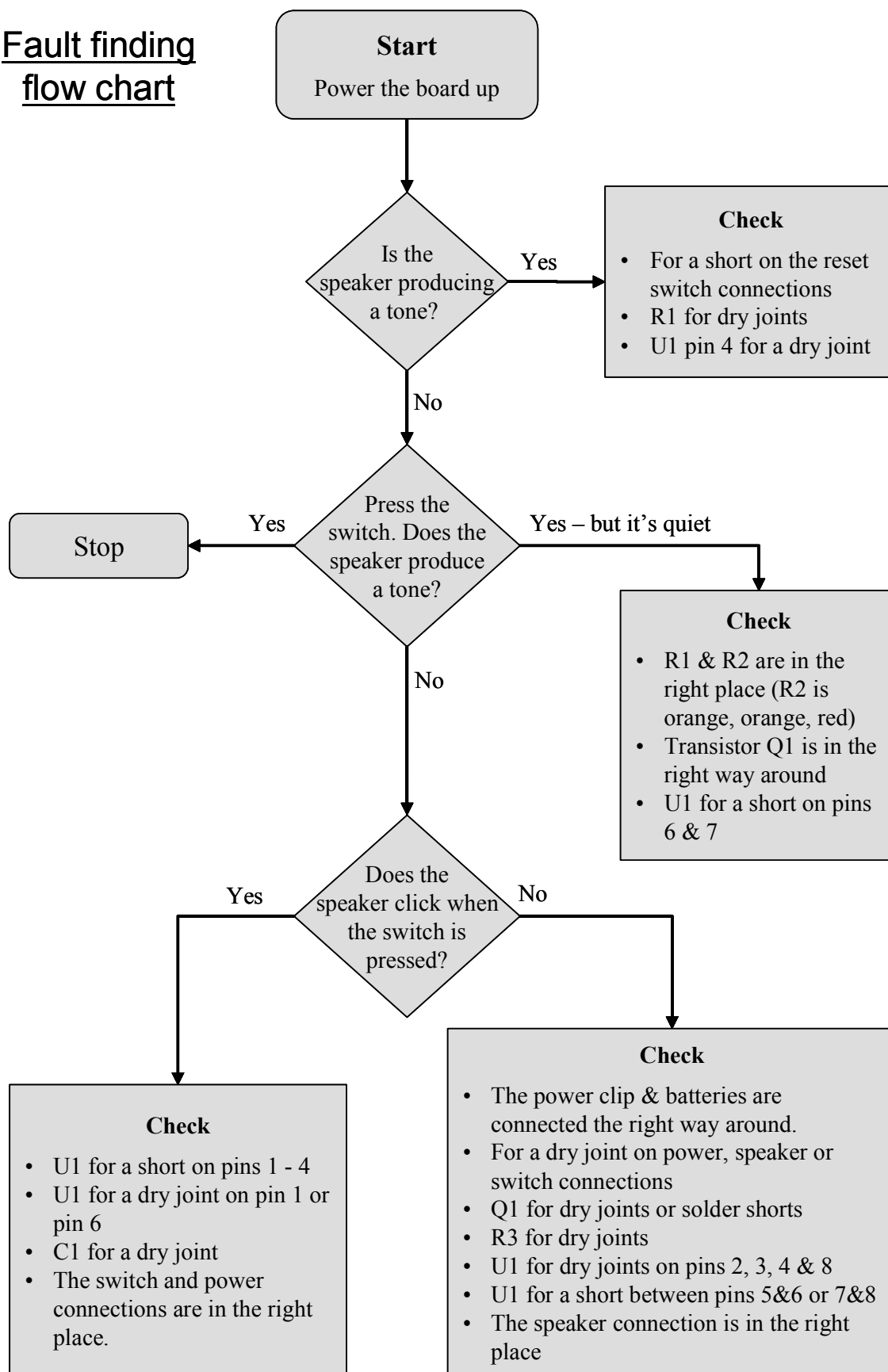

The 555 IC

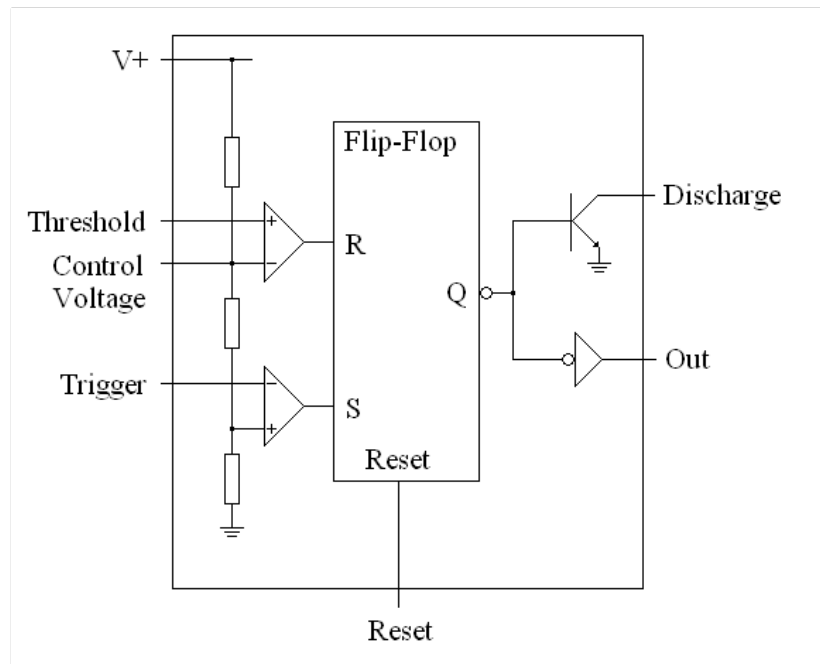

Operating Overview

The 555 Timer is a simple integrated circuit. By taking the trigger signal from high to low, the flip-flop is set. This causes the output to go high and the discharge pin to be released from Gnd (0V). The releasing of the discharge pin from Gnd causes an external capacitor to begin charging.

When the capacitor is charged, the voltage across it increases. This results in the voltage on the threshold pin increasing. When this is high enough it will result in the threshold pin, causing the flip-flop to reset.


This causes the output to go low and the discharge pin is also taken back to Gnd. This discharges the external capacitor, ready for the next time that the device is triggered.

Pin Descriptions

V+	=	Supply voltage.
GND	=	Gnd (0V) connection for supply voltage.
Threshold	=	Active high input pin that is used to monitor the charging of the timing capacitor.
Control Voltage	=	Used to adjust the threshold voltage if required. This should be left disconnected if the function is not required. A 0.01uF capacitor to Gnd can be used in electrically noisy circuits.
Trigger	=	Active low trigger input that start the timer.
Discharge	=	Output pin that is used to discharge the timing capacitor.
Out	=	Timer output pin.
Reset	=	Active low reset pin. Normally connected to V+ if the reset function is not required.



How the Square Wave Generator Works

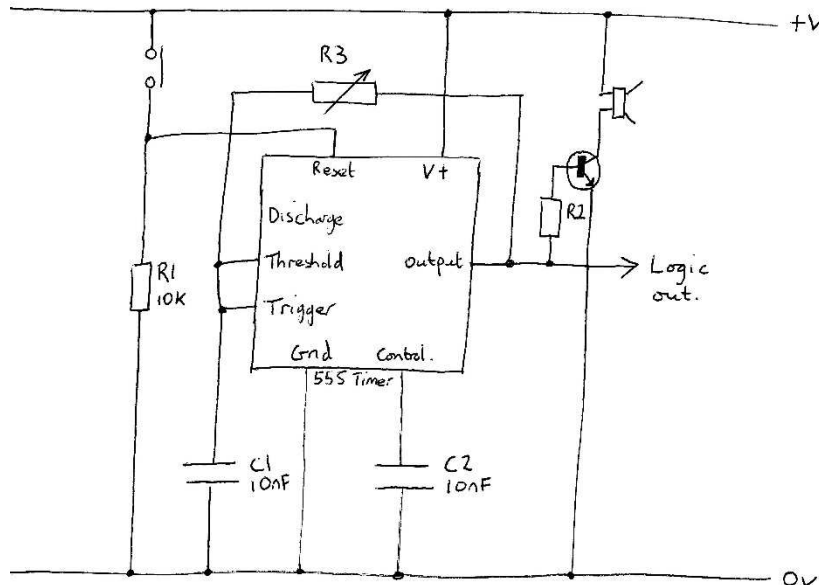

555 timer

The 555 Timer needs to be configured as an astable timer (it outputs a continuous alternating signal). In this configuration the 555 Timer re-triggers itself after each cycle, which results in the continuous alternating signal.

The frequency of the output frequency is determined by the time taken to charge the 10nF capacitor C1. This capacitor charges through the 47K variable resistor R3. When the output of the circuit (pin 3) goes high, C1 begins to charge until the voltage across it is high enough to activate the threshold input. This causes the output to go low and the capacitor now starts to discharge through R3. This continues until the voltage across C1 is low enough to activate the (active low) trigger input. The output now goes high and the process is repeated.

The minimum 555 output frequency is determined as follows:

$$f = \frac{1.44}{R3 \times C1} \quad f = \frac{1.49}{47K \times 10nF} \quad \text{Hence } f \text{ is approx. } 3.2\text{KHz.}$$

The output signal is used to switch the transistor. The transistor is used as it allows larger loads (i.e. the speaker) to be driven than the 555 Timer output could drive on its own.

The reset line is active low, this means that to hold the timer in reset so that the timer stops, the reset line is taken low and in normal operation it is taken high. This is implemented with the 10K pull down resistor R1 and the push to make switch between the reset pin and the supply line. When this buttons is pressed the circuit operates and the tone is generated. When it is released the circuit is held in reset and no tone is generated.

The capacitor C2 on the control voltage (CV) pin is present for improved noise immunity.







Designing the Enclosure


When you design the enclosure, you will need to consider:

- The size of the PCB (below left).
- Where the batteries will be housed.
- Where the switch will be mounted.
- Where the speaker will be mounted (if you are using one).

This technical drawing PCB and other components should help you to design your enclosure.

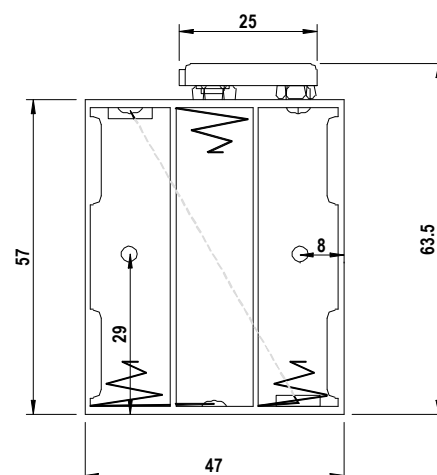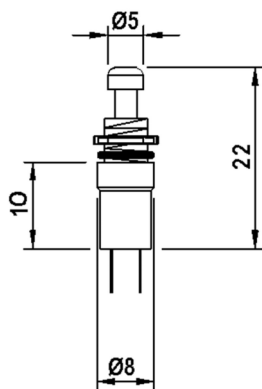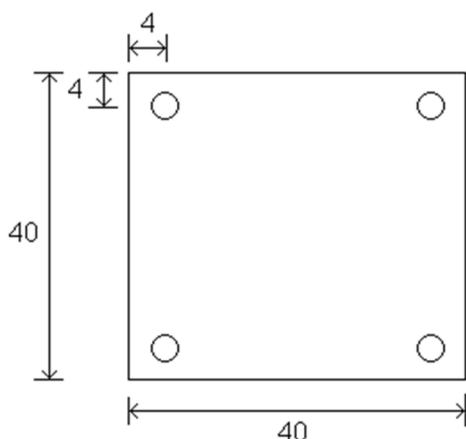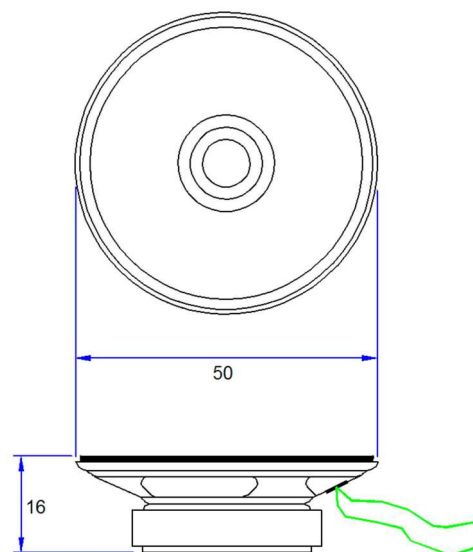All dimensions are in mm. The PCB has four mounting holes 3.3mm in diameter.



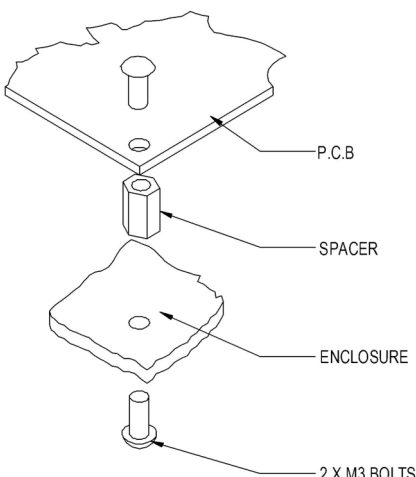	<p>Mounting the PCB to the enclosure</p> <p>The drawing to the left shows how a hex spacer can be used with two bolts to fix the PCB to the enclosure.</p> <p><i>Your PCB has four mounting holes designed to take M3 bolts.</i></p>
---	---



Online Information

Two sets of information can be downloaded from the product page where the kit can also be reordered from. The 'Essential Information' contains all of the information that you need to get started with the kit and the 'Teaching Resources' contains more information on soldering, components used in the kit, educational schemes of work and so on and also includes the essentials. Download from:

www.kitronik.co.uk/2117



This kit is designed and manufactured in the UK by Kitronik

Telephone: +44 (0) 845 8380781

Sales email: sales@kitronik.co.uk

Tech support email: support@kitronik.co.uk

Web: www.kitronik.co.uk



www.kitronik.co.uk/twitter



www.kitronik.co.uk/facebook



www.kitronik.co.uk/youtube



www.kitronik.co.uk/google

Every effort has been made to ensure that these notes are correct, however Kitronik accept no responsibility for issues arising from errors / omissions in the notes.

© Kitronik Ltd - Any unauthorised copying / duplication of this booklet or part thereof for purposes except for use with Kitronik project kits is not allowed without Kitronik's prior consent.

