

Chipsmall Limited consists of a professional team with an average of over 10 year of expertise in the distribution of electronic components. Based in Hongkong, we have already established firm and mutual-benefit business relationships with customers from, Europe, America and south Asia, supplying obsolete and hard-to-find components to meet their specific needs.

With the principle of "Quality Parts, Customers Priority, Honest Operation, and Considerate Service", our business mainly focus on the distribution of electronic components. Line cards we deal with include Microchip, ALPS, ROHM, Xilinx, Pulse, ON, Everlight and Freescale. Main products comprise IC, Modules, Potentiometer, IC Socket, Relay, Connector. Our parts cover such applications as commercial, industrial, and automotives areas.

We are looking forward to setting up business relationship with you and hope to provide you with the best service and solution. Let us make a better world for our industry!



Contact us

Tel: +86-755-8981 8866 Fax: +86-755-8427 6832

Email & Skype: info@chipsmall.com Web: www.chipsmall.com

Address: A1208, Overseas Decoration Building, #122 Zhenhua RD., Futian, Shenzhen, China







Ceramic Resonator (CERALOCK®)



Application Manual



Innovator in Electronics

Murata Manufacturing Co., Ltd.

Introduction

Ceramic resonators (CERALOCK $^{\otimes}$) are made of high stability piezoelectric ceramics that function as a mechanical resonator.

This device has been developed to function as a reference signal generator and the frequency is primarily adjusted by the size and thickness of the ceramic element.

With the advance of the IC technology, various equipment may be controlled by a single LSI integrated circuit, such as the one-chip microprocessor. CERALOCK® can be used as the timing element in most microprocessor based equipment.

In the future, more and more applications will use CERALOCK® because of its high stability non-adjustment performance, miniature size and cost savings. Typical applications include TVs, VCRs, automotive electronic devices, telephones, copiers, cameras, voice synthesizers, communication equipment, remote controls and toys.

This manual describes CERALOCK® and will assist you in applying it effectively.

*CERALOCK® is the brand name of these MURATA products.

1 Characteristics and Types of CERALOCK®	
1. General Characteristics of CERALOCK®	
2. Types of CERALOCK®kHz Band CERALOCK® (CSBLA Series)	
MHz Band CERALOCK® with Built-in Load Capacitance	3
(CSTLS Series)	4
Reflow Solderable kHz Band CERALOCK® (CSBFB Series) MHz Band Chip CERALOCK® (CSACW/CSTCC/ CSTCR/CSTCE/CSTCW Series)	5
2 Principles of CERALOCK®	
1. Equivalent Circuit Constants	
Equivalent Circuit Constants Basic Oscillation Circuits	
3 Specifications of CERALOCK® ————	
1. Electrical Specifications	
Electrical Specifications of kHz Band CSBLA Series	14
Electrical Specifications of MHz Band Lead CERALOCK®	
(CSTLS Series) Electrical Specifications of MHz Band Chip CERALOCK®	15
(CSACW Series) (CSTCC/CSTCR/CSTCE/CSTCW Series)	16
2. Mechanical and Environmental	
Specifications of CERALOCK®	17
4 Applications of Typical Oscillation Circuits	— 19
1. Cautions for Designing Oscillation Circuits	19
2. Application to Various Oscillation Circuits	20
Application to C-MOS Inverter	
Application to H-CMOS Inverter	21
5 Characteristics of	
CERALOCK® Oscillation Circuits —	— 22
1. Stability of Oscillation Frequency	22
2. Characteristics of the Oscillation Level	23
3. Characteristics of Oscillation Rise Time	
4. Starting Voltage	25
6 Application Circuits to Various ICs/LSIs -	— 26
1. Application to Microcomputers	
2. Application to Remote Control ICs	
3. Application to ICs for Office Equipment	
4. Other Kinds of Applications to Various ICs	
7 Notice	90
7 Notice —	— 30
8 Appendix Equivalent Circuit Constants of	

CERALOCK® -

CONTENTS

1	Characteristics and Types of CERALOCK®
2	Principles of CERALOCK®
3	Specifications of CERALOCK®
4	Applications of Typical Oscillation Circuits
5	Characteristics of CERALOCK® Oscillation Circuits
6	Application Circuits to

Appendix Equivalent Circuit Constants of CERALOCK®

Notice

1. General Characteristics of CERALOCK®


Ceramic resonators use the mechanical resonance of piezoelectric ceramics. (Generally, lead zirconium titanate: PZT.)

The oscillation mode varies with resonant frequency. The table on the right shows this relationship. As a resonator device, quartz crystal is well-known. RC oscillation circuits and LC oscillation circuits are also used to produce electrical resonance. The following are the characteristics of CERALOCK®.

- 1) High stability of oscillation frequency Oscillation frequency stability is between that of the quartz crystal and LC or RC oscillation circuits. The temperature coefficient of quartz crystal is 10⁻⁶/°C maximum and approximately 10⁻³ to 10⁻⁴/°C for LC or RC oscillation circuits. Compared with these, it is 10^{-5} /°C at -20 to +80°C for ceramic resonators.
- 2 Small configuration and light weight The ceramic resonator is half the size of popular quartz crystals.
- 3 Low price, non-adjustment CERALOCK® is mass produced, resulting in low cost and high stability. Unlike RC or LC circuits, ceramic resonators use mechanical resonance. This means it is not basically affected by external circuits or by the fluctuation of the supply voltage. Highly stable oscillation circuits can therefore be made without the need of adjustment.

The table briefly describes the characteristics of various oscillator elements.

■Vibration Mode and Frequency Range

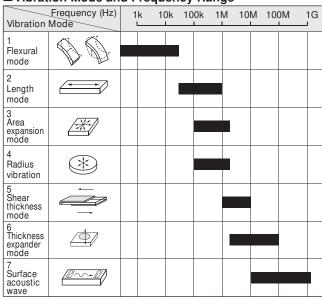

→ show the direction of vibration

■Characteristics of Various Oscillator Elements


Name	Symbol	Price	Size	Adjust- ment	Oscillation Frequency Initial Tolerance	Long-term Stability
LC		Inexpen- sive	Big	Required	±2.0%	Fair
CR	Inexp sive		Small	Required	±2.0%	Fair
Quartz Crystal	o— ∏—∘	Expen- sive	Big	Not required	±0.001%	Excellent
Ceramic Resonator	— П—о	Inexpen- sive	Small	Not required	±0.5%	Excellent



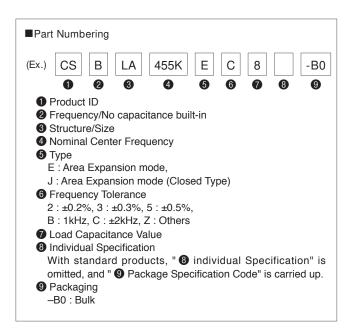2. Types of CERALOCK®

kHz Band CERALOCK® (CSBLA Series)

The CSBLA series uses are a vibration mode of the piezoelectric ceramic element. The dimensions of this element vary with frequency. The ceramic element is sealed in a plastic case and the size of the case also varies with the frequency band. Washable products are available in all the frequencies; however, three standard products (375 to 699kHz) are also made in less expensive non-washable models.



■ Part Numbers and Dimensions of kHz Band CERALOCK® (CSBLA Series) (Standard Products)


CERALOCK®	(CSBLA Series)	(Standard Products)
Part Number	Frequency (kHz)	Dimensions (in mm)
	375–429	7.9
CSBLAE Non-Washable	430–509	7.0
	510–699	7.0
CSBLA J Washable* (Closed Type)	700–1250	2.5 5.0 0.9 1.9 2.5

^{*}Please consult Murata regarding ultrasonic cleaning conditions to avoid possible damage during ultrasonic cleaning.

MHz Band CERALOCK® with Built-in Load Capacitance (CSTLS Series)

As CSTLS series does not require externally mounted capacitors, the number of components can be reduced, allowing circuits to be made more compact.

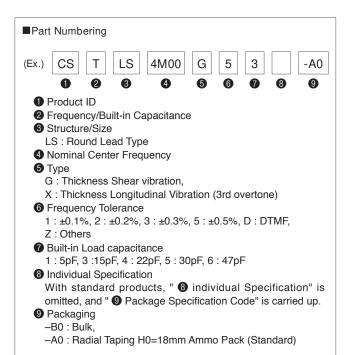The table shows the frequency range and appearance of the three terminal CERALOCK $\mbox{\ensuremath{}^{8}}$ with built-in load capacitance.




■ Part Numbers and Dimensions of CERALOCK® with Built-in Load Capacitance (CSTLS Series)

Built-in Load Capacitance (CSTLS Series)					
Part Number	Frequency	Dimensions (in mm)			
CSTLS.G	3.40–10.00MHz	2.5 2.5			
CSTLS.X	16.00–70.00MHz	2.5 2.5			

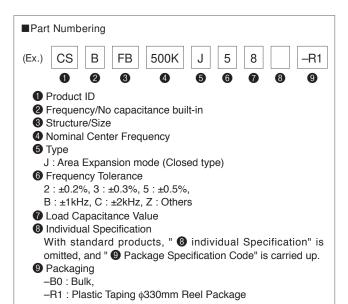* 16.00-32.99MHz : 3.5

Reflow Solderable kHz Band CERALOCK® (CSBFB Series)

Reflow solderable kHz band CERALOCK® (CSBFB series) have been developed to meet down sizing and S.M.T. (Surface Mount Technology) requirements.




■ Dimensions of Reflow Solderable CERALOCK® (CSBFB Series)

Part Number *1	Frequency (kHz)	Dimensions (in mm)
CSBFBJ	430–519	\$50 × 700
CSBFBJ	700–1250°2	25 / F.O

- *1 Please consult Murata regarding ultrasonic cleaning conditions to avoid possible damage during Ultrasonic cleaning.
- *2 Not available for certain frequencies

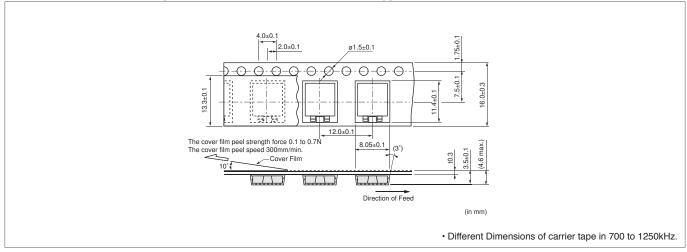■ Dimensions of Carrier Tape for CSBFB Series (430 to 519kHz Type)




MHz Band Chip CERALOCK® (CSACW/CSTCC/CSTCR/CSTCE/CSTCW Series)

The MHz band Chip CERALOCK® has a wide frequency range and small footprint to meet further down sizing and high-density mounting requirements.

The table shows the dimensions and two terminals standard land patterns of the CERALOCK® CSACW series.

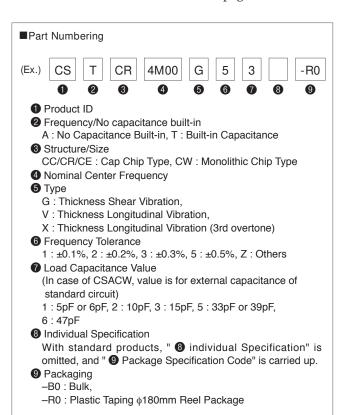The second table shows the dimensions and three terminals standard land patterns of CSTCC/CSTCR/CSTCE/CSTCW series chip resonator (built-in load capacitance type). And the carrier tape dimensions of CSTCR series are shown on the next page.



■Dimensions and Standard Land Pattern of Chip CERALOCK® (CSACW Series)

Part Number	Frequency (MHz)	Dimensions Standard Land Pattern (in mm)
CSACWX	20.01–70.00	0.5 0.5 0.5 0.5 0.5 0.5 0.5 0.5


^{*1} Thickness varies with frequency.

■Dimensions and Standard Land Pattern of Chip CERALOCK® (CSTCC/CSTCR/CSTCE/CSTCW Series)

Part Number	Frequency (MHz)	Dimensions Standard Land Pattern (in mm)
CSTCC G'2	2.00–3.99	25 25
CSTCR G'2	4.00–7.99	0.8, 0.7, 0.8, 0.7, 0.8
CSTCE G'2	8.00–13.99	0.4 0.8 0.4 0.8 0.4
CSTCEV'2	14.00–20.00	0.3, 0.65, 0.3, 0.65, 0.3
CSTCW\X'2	20.01–70.00	0.50.50.50.50.50.50.50.50.50.50.50.50.50



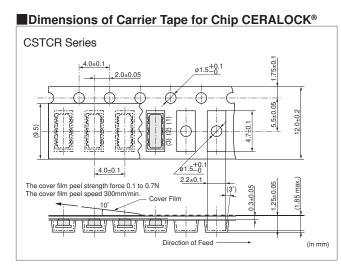^{*1} Thickness varies with frequency
*2 Conformal coating or washing of the components is not acceptable because they are not hermetically sealed.



1. Equivalent Circuit Constants

Fig. 2-1 shows the symbol for a ceramic resonator. The impedance and phase characteristics measured between the terminals are shown in Fig. 2-2. This illustrates that the resonator becomes inductive in the frequency zone between the frequency Fr (resonant frequency), which provides the minimum impedance, and the frequency Fa (anti-resonant frequency), which provides the maximum impedance.

It becomes capacitive in other frequency zones. This means that the mechanical vibration of a two terminal resonator can be replaced equivalently with a combination of series and parallel resonant circuits consisting of an inductor: L, a capacitor: C, and a resistor: R. In the vicinity of the specific frequency (Refer to Note 1 on page 10.), the equivalent circuit can be expressed as shown in Fig. 2-3.

Fr and Fa frequencies are determined by the piezoelectric ceramic material and the physical parameters. The equivalent circuit constants can be determined from the following formulas. (Refer to Note 2 on page 10.)

 $\begin{aligned} &Fr = 1/2\pi \ \sqrt{L_1C_1} & & & & & & & & & & & & \\ &Fa = 1/2\pi \ \sqrt{L_1C_1C_0/(C_1 + C_0)} = &Fr \ \sqrt{1 + C_1/C_0} & & & & & & & & \\ &Qm = 1/2\pi Fr C_1R_1 & & & & & & & & \\ &Qm : Mechanical \ Q) & & & & & & & & \\ \end{aligned}$

Considering the limited frequency range of $Fr \le F \le Fa$, the impedance is given as $Z=Re+j\omega Le$ ($Le \ge 0$) as shown in Fig. 2-4, and $CERALOCK^{\circledast}$ should work as an inductance Le (H) having the loss Re (Ω).

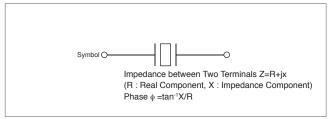


Fig. 2-1 Symbol of the Two Terminal CERALOCK®

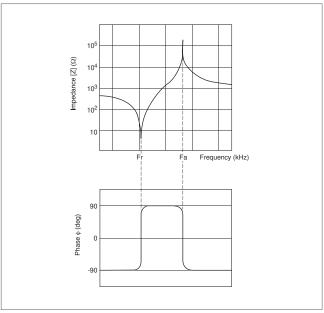


Fig. 2-2 Impedance and Phase Characteristics of CERALOCK®

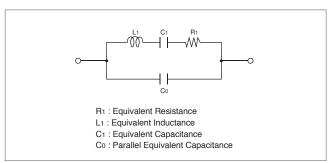


Fig. 2-3 Electrical Equivalent Circuit of CERALOCK®

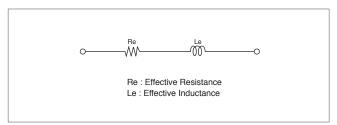


Fig. 2-4 Equivalent Circuit of CERALOCK® in the Frequency Band Fr≦F≦Fa

The table on this page shows comparison for the equivalent constants between CERALOCK and quartz crystal oscillator.

In comparison, there is a large difference in capacitance and Qm, which results in the difference of oscillating conditions, when actually operated.

The table in the appendix shows the standard values of equivalent circuit constant for each type of CERALOCK®. Furthermore, other higher harmonic modes exist, other than the desired oscillation mode. These other oscillation modes exist because the ceramic resonator uses mechanical resonance.

Fig. 2-5 shows those characteristics.

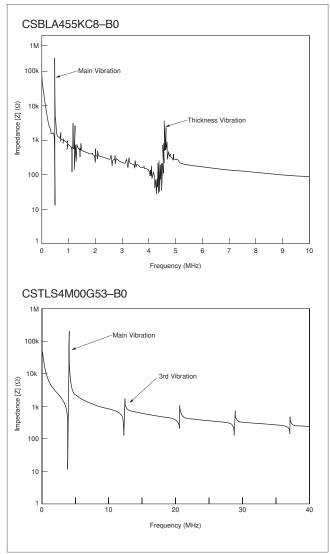


Fig. 2-5 Spurious Characteristics of CERALOCK®

■Comparison of Equivalent Circuits of CERALOCK® and Crystal Oscillator

Comparison of Equivalent Circuits of CERALOCK and Crystal Oscillator							
Resonator	Oscillation Frequency	L1 (μH)	C ₁ (pF)	C ₀ (pF)	R ₁ (Ω)	Qm	dF (kHz)
	455kHz	7.68×10 ³	16.7	272.8	10.1	2136	13
CERALOCK®	2.00MHz	1.71×10³	4.0	20.8	43.9	475	177.2
GENALOGK*	4.00MHz	0.46×10 ³	3.8	19.8	9.0	1220	350.9
	8.00MHz	0.13×10³	3.5	19.9	8.0	775	641.6
	453.5kHz	8.6 ×10 ⁶	0.015	5.15	1060	23000	0.6
Crystal	2.457MHz	7.2 ×10 ⁵	0.005	2.39	37.0	298869	3
Grystai	4.00MHz	2.1 ×10 ⁵	0.007	2.39	22.1	240986	6
	8.00MHz	1.4 ×10 ⁴	0.027	5.57	8.0	88677	19

Notes

(Note 1)

The relationship between the size of the resonator and the resonant frequency is described as follows. For example, the frequency doubles if the thickness doubles, when thickness vibration is used. The following relationship is obtained when the length of the resonators is ℓ , the resonance frequency is Fr, the speed of sound waves travelling through piezoelectric ceramics, and the wavelength is λ .

Fr· ℓ = Const. (frequency constant, Fr·t for the thickness) $\lambda = 2 \ \ell$ $C = Fr \cdot \lambda = 2Fr \cdot \ell$

As seen in the above formula, the frequency constant determines the size of the resonator.

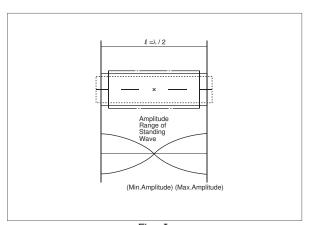


Fig. I

(Note 2)

In Fig. 2-3, when resistance R_1 is omitted for simplification, the impedance $Z\left(\omega\right)$ between two terminals is expressed by the following formula.

$$\begin{split} Z\left(\omega\right) &= \frac{\frac{1}{j\omega C_{0}}(j\omega L_{1} + \frac{1}{j\omega C_{1}})}{\frac{1}{j\omega C_{0}} + (j\omega L_{1} + \frac{1}{j\omega C_{1}})} \\ &= \frac{j\left(\omega L_{1} - \frac{1}{\omega C_{1}}\right)}{1 + \frac{C_{0}}{C_{1}} - \omega^{2} \operatorname{Co}L_{1}} \end{split}$$

When
$$\omega = \frac{1}{\sqrt{\mathrm{L_1C_1}}} = \omega \mathrm{r}, \, \mathrm{Z} \left(\omega \mathrm{r} \right) = 0$$

When
$$\omega = \frac{1}{\sqrt{C_0C_1L_1/(C_0+C_1)}} = \omega a, Z(\omega a) = \infty$$

Therefore from $\omega = 2\pi F$,

$$\mathrm{Fr} = \omega \mathrm{r}/2\pi = \frac{1}{2\pi\sqrt{\mathrm{L}_1\mathrm{C}_1}}$$

Fa =
$$\omega a/2\pi = \frac{1}{2\pi \sqrt{C_0C_1L_1/(C_0+C_1)}} = \text{Fr } \sqrt{1 + \frac{C_1}{C_0}}$$

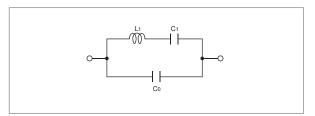


Fig. I

2. Basic Oscillation Circuits

Generally, basic oscillation circuits can be grouped into the following 3 categories.

- ① Use of positive feedback
- 2 Use of negative resistance element
- ③ Use of delay in transfer time or phase In the case of ceramic resonators, quarts crystal oscillators, and LC oscillators, positive feedback is the circuit of choice.

Among the positive feedback oscillation circuit using an LC, the tuning type anti-coupling oscillation circuit, Colpitts and Hartley circuits are typically used. See Fig. 2-6.

In Fig. 2-6, a transistor, which is the most basic amplifier, is used.

The oscillation frequencies are approximately the same as the resonance frequency of the circuit consisting of L, C_{L1} and C_{L2} in the Colpitts circuit or consisting of L_1 and L_2 in the Hartley circuit. These frequencies can be represented by the following formulas. (Refer to Note 3 on page 13.)

(Colpitts Circuit)

fosc.
$$= \frac{1}{2\pi \sqrt{L \cdot \frac{C_{L1} \cdot C_{L2}}{C_{L1} + C_{L2}}}}$$
 (2-4)

(Hartley Circuit)

fosc.
$$=\frac{1}{2\pi \sqrt{C (L_1+L_2)}}$$
 (2-5)

In an LC network, the inductor is replaced by a ceramic resonator, taking advantage of the fact that the resonator becomes inductive between resonant and anti-resonant frequencies.

This is most commonly used in the Colpitts circuit. The operating principle of these oscillation circuits can be seen in Fig. 2-7. Oscillation occurs when the following conditions are satisfied.

Loop Gain
$$G = \alpha \cdot \beta \ge 1$$

Phase Amount (2-6)
 $\theta = \theta + \theta = 360^{\circ} \times n \ (n = 1, 2, \cdots)$

In Colpitts circuit, an inverter of θ 1 = 180° is used, and it is inverted more than θ 2 = 180° with L and C in the feedback circuit. The operation with a ceramic resonator can be considered the same.

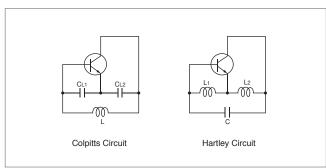


Fig. 2-6 Basic Configuration of LC Oscillation Circuit

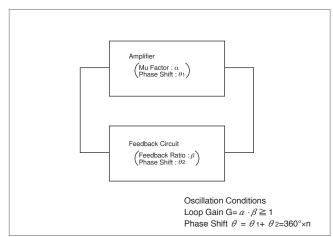


Fig. 2-7 Principle of Oscillation

It is general and simple to utilize inverter for Colpitts circuit with CERALOCK $^{\text{\tiny{\$}}}$.

Fig. 2-8 shows the basic oscillation circuit with inverter. In open loop circuit by cutting at A point, it is possible to measure loop gain G and phase shift θ .

Fig. 2-9 shows the actual measuring circuit, and the example of measuring result is shown in Fig. 2-10.

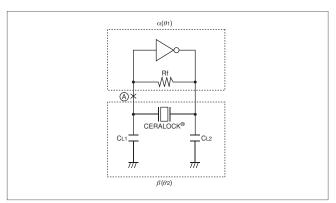


Fig. 2-8 Basic Oscillation Circuit with inverters

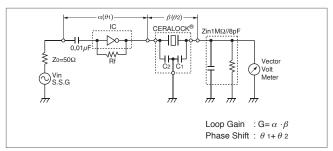


Fig. 2-9 Measuring Circuit Network of Loop Gain and Phase Shift

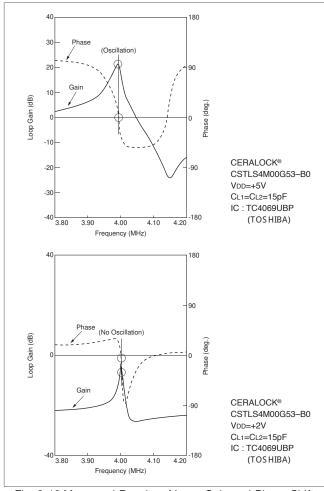


Fig. 2-10 Measured Results of Loop Gain and Phase Shift

Notes

(Note 3)

Fig. III shows the equivalent circuit of an emitter grounding type transistor circuit. In the figure, Ri stands for input impedance, Ro stands for output impedance and B stands for current amplification rate.

When the oscillation circuit in Fig. 2-6 is expressed by using the equivalent circuit in Fig. III , it becomes like Fig. IV . Z_1 , Z_2 and Z are as shown in the table for each Hartley type and Colpitts type circuit.

The following 3 formulas are obtained based on Fig. \mathbb{N} .


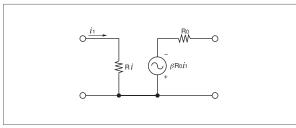


Fig. II

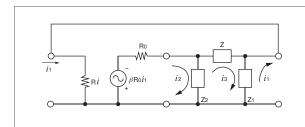

	Hartley Type	Colpitts Type
Z ₁	jωL1	1 / jωC _{L1}
Z ₂	jωL2	1 / jωCL2
Z	1 / jωC	jωL

Fig. IV Hartley/Colpitts Type LC Oscillation Circuits

$$\begin{cases} \beta \text{ Ro}i_1 + (\text{Ro} + \text{Z2}) i_2 - \text{Z2}i_3 = 0 & \cdots & (1) \\ \text{Z}_1i_1 + \text{Z}_2i_2 - (\text{Z2} + \text{Z}_1 + \text{Z1}) i_3 = 0 & \cdots & (2) \\ (\text{Z}_1 + \text{Ri}) i_1 - \text{Z}_1i_3 = 0 & \cdots & (3) \end{cases}$$

As $i_1 \neq 0$, $i_2 \neq 0$, $i_3 \neq 0$ are required for continuous oscillation, the following conditional formula can be performed by solving the formulas of (1), (2) and (3) on the current.

$$\begin{cases} \beta R_0 Z_1 Z_2 = (Z_1 + R_i) Z_2^2 - \{Z_1 (Z_2 + Z) + (Z_2 + Z_1) R_i\} (Z_2 + R_0) & \cdots \end{cases}$$
(4)

Then, as Z_1 , Z_2 and Z are all imaginary numbers, the following conditional formula is obtained by dividing the formula (4) into the real number part and the imaginary number part.

Formula (5) represents the phase condition and formula (6) represents the power condition. Oscillation frequency can be obtained by applying the elements shown in the aforementioned table to Z_1 Z_2 and Z solving it for angular frequency ω . (Hartley Type)

$$\omega^{2} \text{osc} = (2\pi \text{ fosc.})^{2} = \frac{1}{(\text{L}_{1}\text{L}_{2}) \text{ C}\{1 + \frac{\text{L}_{1} \cdot \text{L}_{2}}{(\text{L}_{1} + \text{L}_{2}) \text{ CR}i\text{R}_{0}}\}}$$
......(7

(Colpitts Type) $\omega^{2} \text{osc} = (2\pi \text{ fosc.})^{2} = \frac{1}{L \frac{\text{CL1} \cdot \text{CL2}}{\text{CL1} + \text{CL2}}} \cdot \{1 + \frac{L}{\text{(CL1} + \text{CL2) R}i\text{Ro}}$ (8)

In either circuit, the term in brackets will be 1 as long as $\mathrm{R}i$ and R_0 is large enough. Therefore oscillation frequency can be obtained by the following formula.

(Hartley Type) fosc.
$$=\frac{1}{2\pi\sqrt{(L_1+L_2)C}}$$
 (9)

(Colpitts Type) fosc.
$$=\frac{1}{2\pi\sqrt{L \cdot \frac{C_{L1} \cdot C_{L2}}{C_{L1} + C_{L2}}}} \cdots$$
 (10)

1. Electrical Specifications

The frequency stability of CERALOCK® is between that of crystal and LC or RC oscillators. Temperature stability is ± 0.3 to $\pm 0.5\%$ against initial values within -20 to +80 °C. The initial frequency precision is ±0.5% for standard products. The frequency of the standard CERALOCK® is adjusted by the standard measuring circuit, but the oscillation frequency may shift when used in the actual IC circuit. Usually, if the frequency precision needed for clock signal of a 1 chip microcomputer is approximately ±2 to 3% under working conditions, CERALOCK® standard type can be used in most cases. If exact oscillation frequency is required for a special purpose, Murata can manufacture the ceramic resonator for the desired frequency. The following are the general electrical specifications of CERALOCK[®]. (As for the standard measuring circuit of oscillation frequency, please refer to the next chapter "Application to Typical Oscillation Circuits".)

Electrical Specifications of kHz Band CSBLA Series

Electrical specifications of CSBLA series are shown in the tables. The value of load capacitance (CL1, CL2) and damping resistance (Rd) depend on the frequency. (The initial frequency tolerance of standard CSBLA \square J type is $\pm 0.5\%$ max.)

■Resonant Impedance Specifications of CSBLA Series

Frequency Range (kHz)	Resonant Impedance (Ω max.)
375- 450	20
451- 504	30
505- 799	40
800- 899	60
900–1099	100
1100–1250	120

■Frequency Specifications of CSBLA Series

Item Part Number	Frequency (kHz)	Initial Tolerance of Oscillation Frequency	Temperature Stability of Oscillation Frequency (-20 to +80°C)	Oscillating Frequency Aging	Standard Circuit for Oscillation Frequency
CSBLA Series (with MOS IC/	375–699	±2kHz	±0.3%	±0.3%	VDD IC : CD4069UBE(RCA) (MOS) : TC74HCU04(TOSHIBA) (H-CMOS)
H–CMOS IC)	700–1250	±0.5%	10.5 /6	EU.3 /6	Rd VDD: +5V X: CERALOCK® CL1 X CL2 CL1, CL2, Rd: Depends on frequency (cf. Fig. 4-2, 4-3)

Electrical Specifications of MHz Band Lead CERALOCK® (CSTLS Series)

Electrical specifications of CSTLS series are shown in the tables. Please note that oscillation frequency measuring circuit constants of the CSTLS

G56 series (with H-CMOS IC) depends on frequency.

MHz band three terminal CERALOCK® (CSTLS Series) is built-in load capacitance.

Fig. 3-1 shows the electrical equivalent circuit. The table shows the general specifications of the CSTLS series. Input and output terminals of the three terminal CERALOCK® are shown in the table titled Dimensions of CERALOCK® CSTLS series in Chapter 1 on page 6. But connecting reverse, the oscillating characteristics are not affected except that the frequency has slight lag.

■Resonant Impedance Specifications of **CSTLS/ Series**

Туре	Frequency Range (MHz)	Resonant Impedance (Ω max.)
	3.40 — 3.99	50
CSTLS□G	4.00 — 7.99	30
	8.00 — 10.00	25
	16.00 — 32.99	50
CSTLS□X	33.00 — 60.00	40
	60.01 — 70.00	50

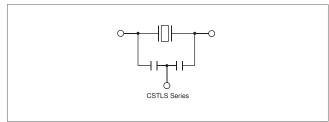


Fig. 3-1 Symbol of the Three Terminal CERALOCK®

■General Specifications CSTLS Series

Part Number	Frequency Range (MHz)	Initial Tolerance Of Oscillation Frequency	Temperature Stability of Oscillation Frequency (-20 to +80°C)	Oscillating Frequency Aging	Standard Circuit for Oscillation Frequency
CSTLS□G53/56	3.40-10.00	±0.5%	±0.2%*1	±0.2%	VDD IC Output
CSTLS□X	16.00-70.00	±0.5%	±0.2%	±0.2%	C : TC4069UBP'3 VDD : +5V X : CERALOCK® Rd : 680Ω'4 Rd : 680Ω

- *1 This value varies for built-in Capacitance
- *2 If connected conversely, there may occur a little frequency lag. *3 G56/X series : TC74HCU04(TOSHIBA), CSTLS series (50.00–70.00MHz) : SN74AHCU04(TI)
- *4 This resistance value applies to the CSTLS \square G56 series.

Electrical Specifications of MHz Band Chip CERALOCK® (CSACW Series) (CSTCC/CSTCR/CSTCE/CSTCW Series)

General specifications of chip CERALOCK® (CSACW series) (CSTCC/CSTCR/CSTCE/CSTCW series) are shown in the tables respectively.

■Resonant Impedance of CSTCC/CSTCR/CSTCE/ CST(A)CW Series

Туре	Frequency Range (MHz)	Resonant Impedance (Ω max.)
CSTCC□G	2.00- 2.99	80
03100 <u></u>	3.00- 3.99	50
CSTCR□G CSTCE□G	4.00- 5.99	60
	6.00- 7.99	50
	8.00-10.00	40
CSTCELLG	10.01-13.99	30
CSTCE□V	14.00-20.00	40
	20.01-24.99	80
CSACW□X/CSTCW□X	25.00-29.99	60
OSAGWENCSTOWEN	30.00-60.00	50
	60.01-70.00	60

■General Specifications of CSACW Series

ltem Part Number	Frequency Range (MHz)	Initial Tolerance of Oscillation Frequency	Temperature Stability of Oscillation Frequency (-20 to +80°C)	Oscillating Frequency Aging	Standard Circuit for Oscillation Frequency
CSACW□ X53	20.01—24.99	±0.5%	±0.2%	±0.1%	IC Output
CSACW□ X51	25.00—70.00	±0.5%	±0.2%	±0.1%	IC: TC74HCU04'(TOSHIBA) VDD: +5V X: Chip CERALOCK® CL1, CL2: This value varies for frequency.

^{*} X51 Series (50.00-70.00MHz); SN74AHCU04

■General Specifications of CSTCC/CSTCR/CSTCE/CSTCW Series

	outions of con-				
Part Number	Frequency Range (MHz)	Initial Tolerance of Oscillation Frequency	Temperature Stability of Oscillation Frequency (-20 to +80°C)	Oscillating Frequency Aging	Standard Circuit for Oscillation Frequency
CSTCC□G	2.00— 3.99	±0.5%	±0.3%*³	±0.3%	Vod
CSTCR□G	4.00— 7.99	±0.5%	±0.2%	±0.1%	IC Output
CSTCE□G	8.00—13.99	±0.5%	±0.2%	±0.1%	
CSTCE□V	14.00-20.00	±0.5%	±0.3%	±0.3%	777 (2)
CSTCW□X	20.01-70.00	±0.5%	±0.2%	±0.1%	IC : TC4069UBP*¹(TOSHIBA) VDD : +5V X : Chip CERALOCK®

^{*1} V, X Series;TC74HCU04(TOSHIBA), X Series (50.00-70.00MHz); SN74AHCU04(TI)

^{*2} If connected with wrong direction, above specification may not be guaranteed.

^{*3} This value varies for built-in Capacitance and Frequency.

$\textbf{Specifications of CERALOCK}^{\text{\tiny{\$}}}$

2. Mechanical and Environmental Specifications of CERALOCK®

The tables show the standard test conditions of mechanical strength and environmental specifications of CERALOCK®.

Fig. 3-2 shows the changes of oscillation frequency in each test, the table on the next page shows the criteria after the tests, and Fig. 3-3 shows the reflow soldering profile.

■Test Conditions for Standard Reliability of CERAL OCK®

Item	Conditions
1. Shock Resistance	Measure after dropping from a height of a cm to b floor surface 3 times.
2. Soldering Heat Resistance	Lead terminals are immersed up to 2.0 mm from the resonator's body in solder bath of, and then the resonator shall be measured after being placed in natural condition for 1 hour. The Reflow profile show in Fig. 3-5 of heat stress is applied to the resonator, then being placed in natural condition for 1 hour, the resonator shall be measured. The resonator shall be measured.
3. Vibration Resistance	Measure after applying vibration of 10 to 55Hz amplitude of 2 mm to each of 3 directions, X, Y, Z.
4. Humidity Resistance	Keep in a chamber with temperature of d and humidity of 90 to 95% for e hours. Leave for 1 hour before measurement.
5. Storage at High Temperature	Keep in a chamber at 85±2°C for e hours. Leave for 1 hour before measurement.
6. Storage at Low Temperature	Keep in a chamber at f °C for e hours. Leave for 1 hour before measurement.
7. Temperature Cycling	Keep in a chamber at -55°C for 30 minutes. After leaving at room temperature for 15 minutes, keep in a chamber at +85°C for 30 minutes, and then room temperature for 15 minutes. After 10 cycles of above, measure at room temperature.
8. Terminal Strength	Apply 1 kg of static load vertically to each terminal and measure.

1. CSBLA Series

Туре	fosc.	а	b	С	d	е	f
J	700—1250kHz	100	concrete	350±10°C	60±2°C	1000	−55±2°C
Е	375— 699kHz	75	concrete	350±10°C	40±2°C	500	-25±2°C

2. CSTLS Series

Type	fosc.	а	b	С	d	е	f
G	3.40-10.00MHz	100	concrete	350±10°C	60±2°C	1000	-55±2°C
Х	16.00-70.00MHz	100	concrete	350±10°C	60±2°C	1000	-55±2°C

3. CSACW Series

Type	fosc.	а	b	С	d	е	f
X	20.01-70.00MHz	100	wooden plate	_	60±2°C	1000	-55±2°C

4. CSTCC/CSTCR/CSTCE/CSTCW Series

Type	fosc.	а	b	С	d	е	f
G	2.00-13.99MHz	100	wooden plate	_	60±2°C	1000	−55±2°C
V	14.00-20.00MHz	100	wooden plate	_	60±2°C	1000	-55±2°C
Х	20.01-70.00MHz	100	wooden plate	_	60±2°C	1000	-55±2°C

^{*1} Applies to CERALOCK® Lead Type *2 Applies to MHz Band Chip CERALOCK®

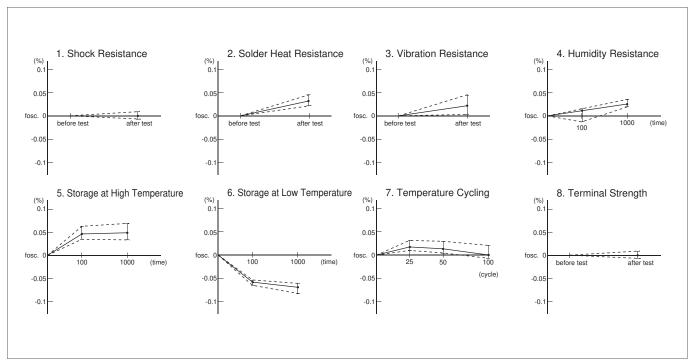


Fig. 3-2 General Changes of Oscillation Frequency in Each Reliability Test (CSTLS4M00G53-B0)

■Deviation after Reliability Test

		•	
7	ltem Type	Oscillation Frequency	Others
E	Every Series	within±0.2%* (from initial value)	Meets the individual specification of each product.

* CSTCC Series : within±0.3%

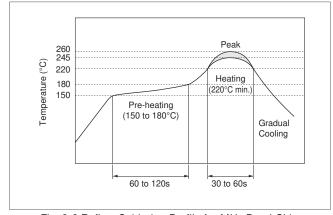


Fig. 3-3 Reflow Soldering Profile for MHz Band Chip CERALOCK®

4

Applications of Typical Oscillation Circuits

As described in Chapter 2, the most common oscillation circuit with CERALOCK® is to replace L of a Colpitts circuit with CERALOCK®. The design of the circuit varies with the application and the IC being used, etc. Although the basic configuration of the circuit is the same as that of a quartz crystal, the difference in mechanical Q results in the difference of the circuit constant.

This chapter briefly describes the characteristics of the oscillation circuit and gives some typical examples.

1. Cautions for Designing Oscillation Circuits

It is becoming more common to configure the oscillation circuit with a digital IC, and the simplest way to use an inverter gate.

Fig. 4-1 shows the configuration of a basic oscillation circuit with a C-MOS inverter.

INV. 1 works as an inverter amplifier of the oscillation circuit. INV. 2 acts to shape the waveform and also acts as a buffer for the connection of a frequency counter. The feedback resistance Rf provides negative feedback around the inverter in order to put it in the linear region, so the oscillation will start, when power is applied.

If the value of Rf is too large, and if the insulation resistance of the input inverter is accidentally decreased, oscillation will stop due to the loss of loop gain. Also, if Rf is too great, noise from other circuits can be introduced into the oscillation circuit. Obviously, if Rf is too small, loop gain will be low. An Rf of $1M\Omega$ is generally used with a ceramic resonator.

Damping resistor Rd provides loose coupling between the inverter and the feedback circuit and decreases the loading on the inverter, thus saving energy.

In addition, the damping resistor stabilizes the phase of the feedback circuit and provides a means of reducing the gain in the high frequency area, thus preventing the possibility of spurious oscillation.

Load capacitance C_{L1} and C_{L2} provide the phase lag of 180°.

The proper selected value depends on the application, the IC used, and the frequency. If C_{L1} and C_{L2} values are too low, the loop gain in the high frequency is increased, which in turn increases the probability of spurious oscillation.

This is particularly likely around 4 to 5 MHz, where the thickness vibration mode lies, as shown in Fig. 2-5 when using kHz band resonator.

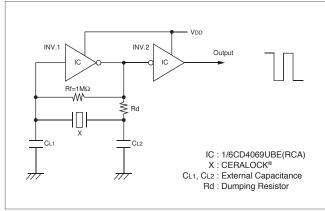


Fig. 4-1 Basic Oscillation Circuit with C-MOS Inverter

4 Application to Typical Oscillation Circuit

Oscillation frequency fosc. in this circuit is expressed approximately by the following equation.

fosc.=Fr
$$\sqrt{1 + \frac{C_1}{C_0 + C_L}}$$
 (4-1)

Where, Fr=Resonance frequency of CERALOCK®

 C_1 : Equivalent series capacitance of $CERALOCK^{\otimes}$

 C_0 : Equivalent parallel capacitance of $CERALOCK^{\circledast}$

$$C_{L=} \ \frac{C_{L1} \ C_{L2}}{C_{L1} + C_{L2}}$$

This clearly shows that the oscillation frequency is influenced by the loading capacitance. And caution should be paid in defining its value when a tight tolerance of oscillation frequency is required.

2. Application to Various Oscillation Circuits

Application to C-MOS Inverter

For the C-MOS inverting amplifier, the one-stage 4069 C-MOS group is best suited.

The C-MOS 4049 type is not used, because the three-stage buffer type has excessive gain, which causes RC oscillation and ringing.

Murata employs the RCA (HARRIS) CD4069UBE as a C-MOS standard circuit. This circuit is shown in Fig. 4-2. The oscillation frequency of the standard CERALOCK® (C-MOS specifications) is adjusted by the circuit in Fig. 4-2.

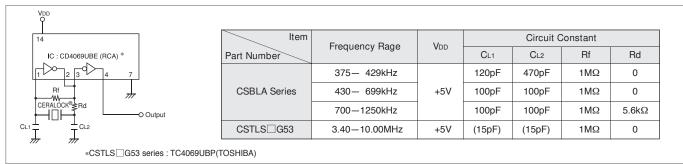


Fig. 4-2 C-MOS Standard Circuit

This PDF catalog has only typical specifications because there is no space for detailed specifications. Therefore, please approve our product specifications or transact the approval sheet for product specifications before ordering.


Application to Typical Oscillation Circuit 4

Application to H-MOS Inverter

Recently, high speed C-MOS (H-CMOS) have been used more frequently for oscillation circuits allowing high speed and energy saving control for the microprocessor. There are two types of H-CMOS inverters: the unbuffered 74HCU series and the 74HC series with buffers.

The 74HCU system is optimum for the CERALOCK® oscillation circuit.

Fig. 4-3 shows our standard H-CMOS circuit. Since H-CMOS has high gain, especially in the high frequency area, greater loading capacitor (CL) and damping resistor (Rd) should be employed to stabilize oscillation performance. As a standard circuit, we recommend Toshiba's TC74CU04, but any 74HCU04 inverter from other manufacturers may be used. The oscillation frequency for H-CMOS specifications is adjusted by the circuit in Fig. 4-3.

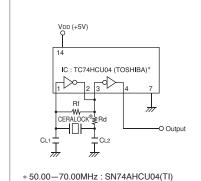

Item	Frequency Rage		Circuit C	Constant	
Part Number	rrequency hage	CL1	CL2	Rf	Rd
0001475(1)	375~ 429kHz	330pF	330pF	1ΜΩ	5.6kΩ
	430~ 699kHz	220pF	220pF	1ΜΩ	5.6kΩ
CSBLA□E (J)	700~ 999kHz	150pF	150pF	1ΜΩ	5.6kΩ
	1000~1250kHz	100pF	100pF	1ΜΩ	$5.6 k\Omega$
CSTLS□G56	3.40~10.00MHz	(47pF)	(47pF)	1ΜΩ	680Ω

Fig. 4-3 H-CMOS Standard Circuit

Characteristics of CERALOCK® Oscillation Circuit

This chapter describes the general characteristics of the basic oscillation of Fig. 4-1 (page. 19). Contact Murata for detailed characteristics of oscillation with specific kinds of ICs and LSIs.

1. Stability of Oscillation Frequency

Fig. 5-1 shows examples of actual measurements for stability of the oscillation frequency.

The stability versus temperature change is ± 0.1 to 0.5% within a range of -20 to +80°C, although varies slightly depending on the ceramic material.

Influence of load capacitance (CL1, CL2) on the oscillation frequency is relatively high, as seen in formula (4-1) (P.20). It varies approximately $\pm 0.05\%$ for a capacitance deviation of $\pm 10\%$. The stability versus supply voltage is normally within $\pm 0.05\%$ in the working voltage range, although it varies with the characteristics of the IC.

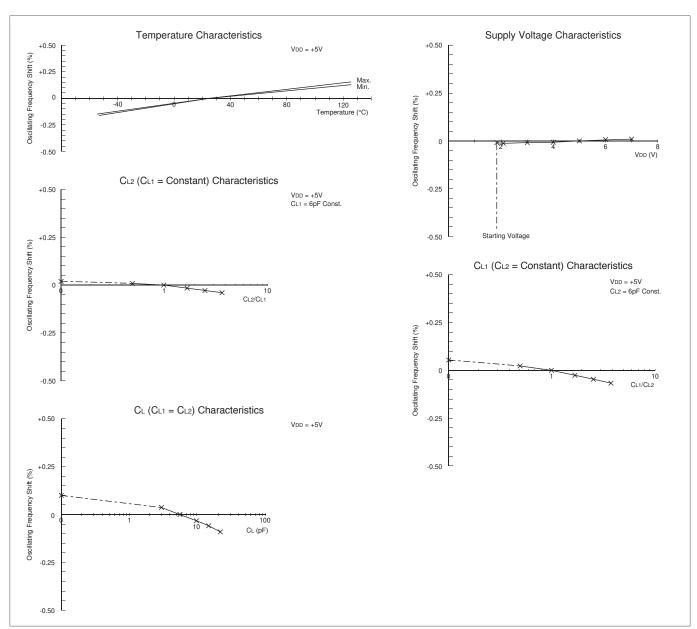


Fig. 5-1 Examples of Actual Measurement for the Stability of Oscillation Frequency (IC: TC74HCU04(TOSHIBA), CERALOCK®: CSACW33M8X51-B0)

Characteristics of CERALOCK® Oscillation Circuit 5

2. Characteristics of the Oscillation Level

Fig. 5-2 shows examples of actual measurements of the oscillation level versus temperature, supply voltage and load capacitance (CL1, CL2). The oscillating amplitude is required to be stable over a wide temperature range, and temperature characteristics should be as flat as possible. The graph titled Supply Voltage Characteristics in Fig. 5-2 shows that the amplitude varies linearly with supply voltage, unless the IC has an internal power supply voltage regulator.

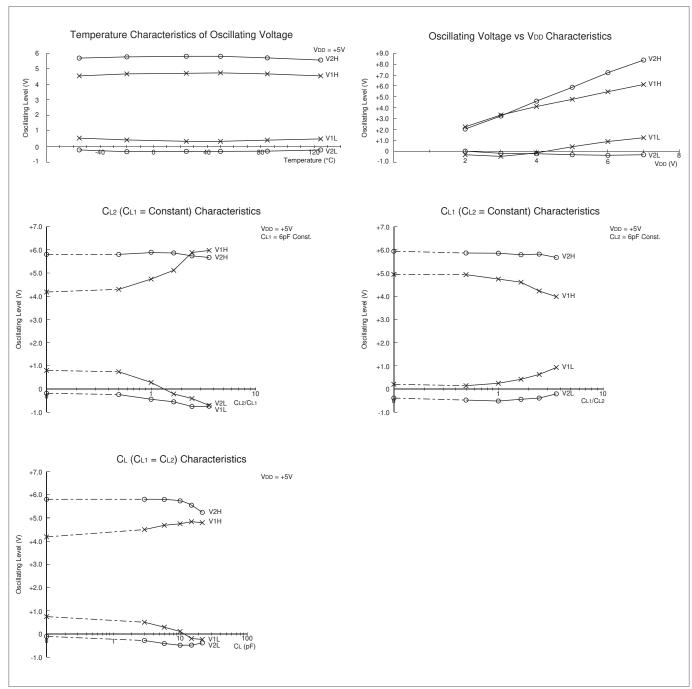


Fig. 5-2 Examples of Actual Measurement of Oscillating Amplitude (IC: TC74HCU04(TOSHIBA), CERALOCK®: CSACW33M8X51–B0)