



Chipsmall Limited consists of a professional team with an average of over 10 year of expertise in the distribution of electronic components. Based in Hongkong, we have already established firm and mutual-benefit business relationships with customers from,Europe,America and south Asia,supplying obsolete and hard-to-find components to meet their specific needs.

With the principle of “Quality Parts,Customers Priority,Honest Operation,and Considerate Service”,our business mainly focus on the distribution of electronic components. Line cards we deal with include Microchip,ALPS,ROHM,Xilinx,Pulse,ON,Everlight and Freescale. Main products comprise IC,Modules,Potentiometer,IC Socket,Relay,Connector.Our parts cover such applications as commercial,industrial, and automotives areas.

We are looking forward to setting up business relationship with you and hope to provide you with the best service and solution. Let us make a better world for our industry!



Contact us

Tel: +86-755-8981 8866 Fax: +86-755-8427 6832

Email & Skype: info@chipsmall.com Web: www.chipsmall.com

Address: A1208, Overseas Decoration Building, #122 Zhenhua RD., Futian, Shenzhen, China



Application Note AN-1169

IRPLLED5 40V/1.4A Low Voltage LED Driver using IRS2548D

By Peter B. Green

Table of Contents

| | Page |
|---|-------------|
| 1. Introduction..... | 2 |
| 2. PFC Section..... | 3 |
| 3. LLC Resonant Half Bridge Section..... | 8 |
| 4. Transformer and Resonant Circuit Design..... | 15 |
| 5. IRPLLED5 Board Schematics..... | 23 |
| 6. Auxiliary VCC Supply..... | 27 |
| 7. Magnetic Specifications..... | 28 |
| 8. Output Current Regulation..... | 31 |
| 9. 0 to 10V Dimming..... | 32 |
| 10. Test Results | 33 |
| 11. Bill of Materials | 37 |
| 12. PCB Layout | 39 |

EVALUATION BOARD - IRPLLED5



1. Introduction

Solid state light sources are now available that offer viable alternatives to Fluorescent and HID lamps and far surpass incandescent lamps. Luminous efficacy expressed in Lumens per Watt has now reached levels enabling LEDs to be used for general illumination. High brightness LEDs also possess the added advantages of longer operating life span up to 50000 hours and greater robustness than other less efficient light sources making them suitable for outside applications such as street lighting.

High power LEDs are ideally driven with constant regulated DC current, requiring a "driver" or "converter" to provide the required current from an AC or DC power source. A two stage power converter based around the IRS2548D PFC plus half bridge LED driver IC provides a controlled current output over a wide AC line voltage input range with high power factor and low THD.

The IRPLLED5 evaluation board is an off line isolated low voltage / high output current LED driver designed to supply a 1.4A regulated DC output current over a voltage range of 30V to 60V operating from an AC line input voltage between 90 and 305VAC 50/60Hz. It also includes 1-10V dimming capability from 0 to 100% of light output. The outputs of this LED driver are fully protected against short circuit and limit the open circuit voltage to below 60VDC for safety compliance.

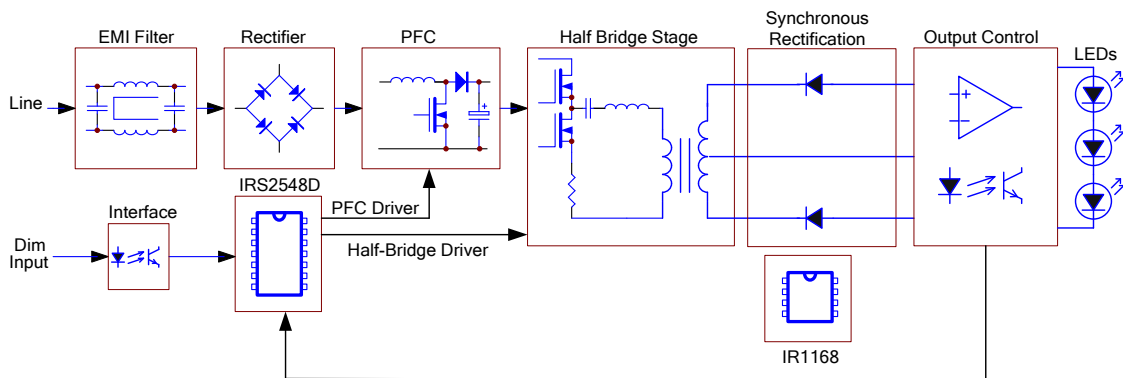


Figure 1: IRPLLED5 Block Diagram

2. PFC Section

The IRPLLED5 board includes a power factor correction Boost converter front end stage, which operates in critical conduction mode. During each switching cycle of the PFC MOSFET the IRS2548D detects the point at which the inductor current has discharged to zero thereby detecting when the stored energy has been completely transferred to the output. The PFC MOSFET is then turned on to start the next switching cycle.

 


Figure 2: PFC Boost converter circuit.

When the switch MPFC is turned on the inductor LPFC is connected between the rectified line input (+) and (-) return causing the current in LPFC to rise linearly. When MPFC is turned off LPFC current is redirected from the rectified line input (+) bus to the DC bus capacitor CBUS through diode DPFC. The stored energy in LPFC is thereby transferred to CBUS. MPFC is switched on and off at a high frequency and the voltage on CBUS charges to a defined voltage. The PFC feedback loop of the IRS2548D regulates this voltage to by continuously monitoring the DC bus voltage and adjusting the on-time of MPFC accordingly. Negative feedback control is performed by a transconductance error amplifier (OTA) with a slow loop speed such that the average inductor current smoothly follows the low frequency line input voltage. This produce a sinusoidal input current yielding high power factor and low THD. The on-time of MPFC is therefore effectively constant (with an additional modulation to be discussed later) only changing over several cycles of the line voltage. With fixed on-time and off-time determined by the inductor current discharging to zero the switching frequency changes from a high frequency near the zero crossing of the AC input line voltage to a lower frequency at the peaks (Figure 3).

 


Figure 3: Sinusoidal line input voltage (solid line), triangular PFC Inductor current and smoothed sinusoidal line input current (dashed line) over one half-cycle of the AC line.

When the line input voltage is low close to the zero crossing, the inductor current also rises to a relatively low peak so the discharge time is also shorter resulting in a high switching frequency. When the input line voltage is high near the peak the inductor current rises to a much higher peak and the discharge time is therefore longer resulting in a lower switching frequency. The PFC control circuit of the IRS2548D (Figure 4) includes five control pins: VBUS, COMP, ZX, PFC and OC. The VBUS pin measures the DC bus voltage via an external resistor voltage divider. The COMP pin voltage at the error amplifier output sets the on-time of and the speed of the feedback loop with an external capacitor. The ZX (zero crossing) pin detects when the inductor current discharges to zero during the off time using a secondary winding from the PFC inductor. The PFC pin is the gate driver output for the external MOSFET, MPFC and the OC pin senses the current flowing through MPFC providing cycle-by-cycle over-current protection.

 


Figure 4: IRS2548D simplified PFC control circuit.

The VBUS pin is regulated against a fixed internal 4V reference voltage for regulation of the output DC bus voltage (Figure 5). The feedback loop error amplifier sinks or sources a current to the external capacitor at the COMP pin. The IRS2548D PFC section operates in voltage mode with the COMP pin voltage providing the threshold for the charging the internal timing capacitor (C1, Figure 5) to control the on-time of MPFC.

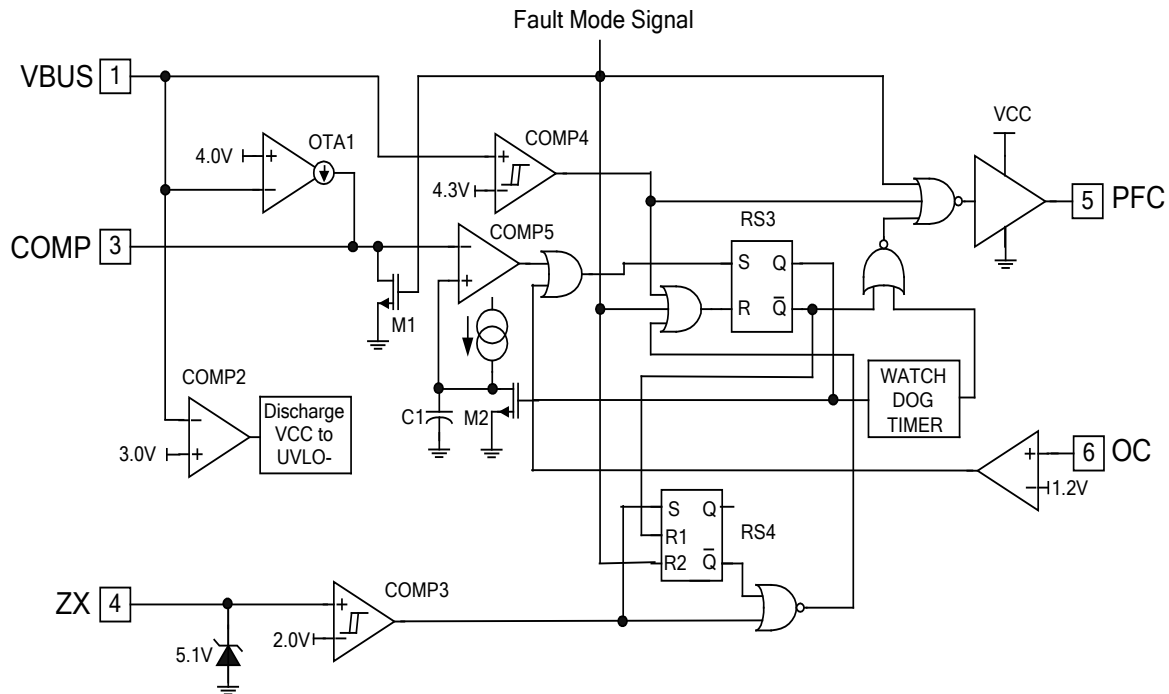


Figure 5: IRS2548D detailed PFC control circuit.

The zero current level is detected by a secondary winding on LPFC connected to the ZX pin through an external current limiting resistor RZX. A positive-going edge exceeding the internal 2V threshold (VZXTH+) signals the beginning of the off-time. A negative-going edge on the ZX pin falling below 1.7V (VZXTH+ - VZXHYS) will occur when the LPFC current discharges to zero, which signals the end of the off-time and MPFC is turned on again (Figure 6). The cycle repeats itself indefinitely until the PFC section is disabled due to a fault detected by the half-bridge driver section (Fault Mode), an over-voltage or condition on the DC bus or the negative transition of ZX pin voltage does not occur. Should the negative edge on the ZX pin fail to be detected for any reason MPFC will remain off until the internal “watch-dog” timer forces a restart. Watch-dog pulses occur every 400us (tW) until a correct positive and negative-going signal is detected on the ZX pin and normal PFC operation is resumed. Should the OC pin exceed the 1.2V (VOCTH+) over-current threshold during the on-time, the PFC output will turn off. The circuit will then wait for a negative-going transition on the ZX pin or a forced turn-on from the watch-dog timer to turn the PFC output on again.

 


Figure 6: Inductor current, PFC pin, ZX pin and OC pin timing diagram.

A fixed on-time of MPFC over an entire cycle of the line input voltage produces a peak inductor current that naturally follows the sinusoidal shape of the line input voltage. The smoothed averaged line input current is in phase with the line input voltage to provide a high power factor. Some harmonic distortion of the line current still remains mostly due to cross-over distortion near the zero-crossings. To achieve low THD additional on-time modulation circuit is built into the IRS2548D PFC control. This function dynamically increases the on-time of MPFC as the line input voltage nears the zero-crossings (Figure 7). This causes the peak LPFC current, and therefore the smoothed line input current, to increase slightly higher near the zero-crossings of the line input voltage.

 


Figure 7: On-time modulation circuit timing diagram

Should over-voltage occur on the DC bus and the VBUS pin exceed the internal 4.3V threshold (VBUSOV+) the PFC output will transition to switch off MPFC.

When the DC bus decreases again and the VBUS pin voltage decreases below the internal 4.15V threshold (VBUSOV-) PFC operation is resumed.

The PFC inductor value can be calculated from the following formula:

$$L_{PFC} = \frac{(VBUS - \sqrt{2} \cdot VAC_{MIN}) \cdot VAC_{MIN}^2 \cdot \eta}{2 \cdot f_{MIN} \cdot P_{OUT} \cdot VBUS} \quad [\text{Henries}]$$

where,

| | |
|-------------|---|
| $VBUS$ | = DC bus voltage |
| VAC_{MIN} | = Minimum RMS AC input voltage |
| η | = PFC efficiency (typically 0.95) |
| f_{MIN} | = Minimum PFC switching frequency at minimum AC input voltage |
| P_{OUT} | = System output power |

The peak current in the PFC inductor is given by:

$$i_{PK} = \frac{2 \cdot \sqrt{2} \cdot P_{OUT}}{VAC_{MIN} \cdot \eta} \quad [\text{Amps Peak}]$$

The PFC inductor should be designed so that it does not saturate at i_{PK} at maximum operating temperature. This involves adequate sizing of the core and air-gap.

The value of the PFC current sense resistor (ROC) is calculated from the following formula and rounded up to the nearest preferred value.

$$R_{OC} = \frac{1.25}{i_{PK}} \quad \text{where } VCSTH+ = 1.25V \quad [\text{Ohms}]$$

3. LLC Resonant Half Bridge Section

The run frequency is programmed with the timing resistor RFMIN at the FMIN pin.

The graph in Figure 6 (RFMIN vs. Frequency) can be used to select RFMIN value for desired run frequency.

 


Figure 8: Graph of frequency against RFMIN

The maximum current is programmed with the external resistor RCS and an internal threshold of 1.25V (VCSTH+). This threshold determines the over-current limit of the system:

$$I_{MAX} = \frac{1.25}{R_{CS}} \quad [\text{Amps Peak}]$$

or

$$R_{CS} = \frac{1.25}{I_{MAX}} \quad [\text{Ohms}]$$

The half-bridge LLC resonant converter offers high efficiency due to zero voltage switching operation which also eliminates switching noise. Since the switching losses are negligible no heat sinking is required for the half-bridge MOSFETs. This topology can achieve high power density due to the efficient utilization of the transformer operating in two quadrants of the B-H curve. The resonant topology requires an additional series inductance to be added to the circuit in order to construct a complex resonant tank with Buck-Boost transfer characteristics in the soft switching region. Although it is possible to incorporate this additional

inductance into the transformer, for simplicity the IRPLLED5 design uses a standard transformer design with the additional inductance added externally. The typical power stage schematic for this topology is shown in figure 9.

 


Figure 9: Typical schematic of a DC-DC half-bridge resonant converter

The half-bridge switches operate at 50% duty cycle where the output voltage is regulated by varying the switching frequency. Since the IRPLLED5 drives an LED load which can be approximately represented by a voltage source with a series resistor. The current is regulated by adjusting the half-bridge switching frequency. The frequency is adjusted to provide the required drive current for varying numbers of LEDs connected to the output up to a total series voltage of 60V. The LLC half-bridge stage has two resonant frequencies, the first determined by the series inductor (L_r) and resonant capacitor (C_r) and the second determined by the transformer magnetizing inductance (L_m) and the resonant capacitor. While the frequency remains in the inductive region soft switching will occur.

 


Figure 10: Typical frequency response of an LLC resonant converter

The characteristics of an LLC resonant converter can be divided into three regions based on the three different modes of operation. The first region is for switching frequency above the resonant frequency F_{r1} :

$$F_{r1} = \frac{1}{2\pi\sqrt{L_r \cdot C_r}}$$

In region 1 of figure 10 (the purple shaded area) the switching frequency is higher than resonant frequency F_{r1} . The converter operation is very similar to a series resonant converter. Here L_m never resonates with resonant capacitor (C_r) it is clamped by the output voltage and acts as the load of the series resonant tank. This is the inductive load region and the converter is always under ZVS operation regardless of the load condition.

In region 2 (the pink shaded area) the switching frequency is higher than the lower resonant frequency but lower than F_{r1} . The lower resonant frequency varies with load so the boundary of region 2 and region 3 traces the peak of the family load vs gain curves. In this complex region the LLC resonant operation can be divided into two time intervals; in the first time interval L_r resonates with C_r and L_m and is clamped by output voltage. When the current in the resonant inductor L_r resonates back to the same level as the magnetizing current L_r and C_r stop resonating. L_m now participates in the resonant operation and the second time interval begins. During this time interval the dominant resonant components become C_r and L_m in series with L_r . The ZVS operation in region 2 is guaranteed by operating the converter to the right side of the load gain curve. For a switching frequency below resonant F_{r1} it could fall in either region 2 or region 3 depending on the load condition.

In the ZCS range below f_{r1} , the LLC resonant converter operates in capacitive mode; M1 and M2 are hard switching with high switching losses. For this reason ZCS operation should always be avoided.

The waveforms in figures 11,12 and 13 show the behavior of the system in each of the operating regions. The typical voltage conversion ratio of a LLC resonant converter is shown in Figure 12.

 


Figure 11: Typical waveform of above resonant ZVS switching

 


Figure 12: Typical waveform of below resonant ZVS switching

The waveforms in figure 12 indicate that the secondary rectifier diode currents move from continuous current mode (CCM) to discontinuous current mode (DCM) when the switching frequency changes from above resonant ZVS to below resonant ZVS due to load increasing. The ripple voltage on the resonant capacitor C_r also increases in the below resonant ZVS mode.

 


Figure 13: Typical waveform of below resonant ZCS switching

In ZCS mode, the two switching devices M1 and M2 are turned off under zero current condition. The turn-on of the two switches is hard switched (non-ZVS). The turn-on switching loss is high especially under high voltage bus voltage. The resonant capacitor C_r also has high voltage stress. ZCS operation should always be avoided.

 


Figure 14: Typical voltage conversion ratio of a LLC resonant converter

With a regulated DC bus voltage supplied from the PFC stage the converter switching frequency can be adjusted to regulate the output voltage and current over the load range keeping the same conversion ratio over the family of curves with different Q. Given a fixed load the converter adjusts the switching frequency along the corresponding load line to regulate the output over input voltage range.

The procedure used to design the LLC resonant half-bridge converter uses the First Harmonic Approximation (FHA) to obtain an equivalent circuit model. All the components are moved to the primary side to simplify analysis. R_{ac} represents the equivalent load resistance in parallel with transformer primary inductance L_m .

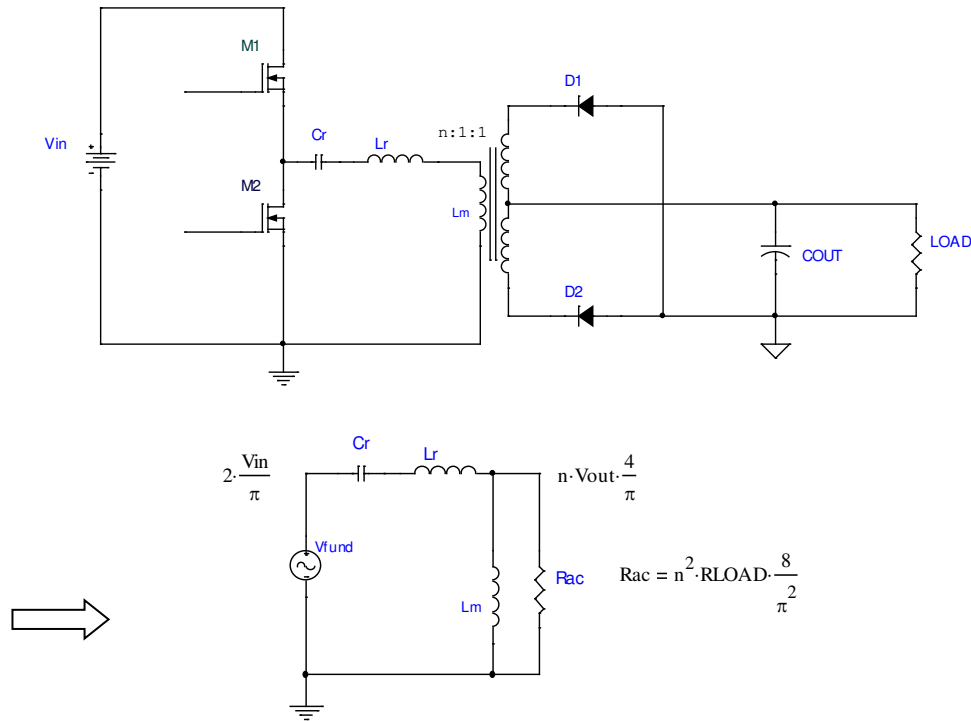


Figure 15: The FHA equivalent circuit

The input voltage of the resonant tank is a square wave with amplitude equal to the DC bus voltage V_{bus} . The fundamental component of the square waveform is:

$$\frac{2 \cdot V_{bus}}{\pi} \sin(\omega \cdot t)$$

The output voltage of the resonant tank is the voltage across L_m . It is very close to a square wave with amplitude swinging from $-n \cdot V_{out}$ to $+n \cdot V_{out}$. So the fundamental component of the output square waveform is:

$$\frac{4 \cdot n \cdot V_{out}}{\pi} \sin(\omega \cdot t)$$

The power dissipation on the equivalent AC resistor is equal to the power dissipation of the load represented by a resistor R_{LOAD} , which can be derived by dividing the maximum output voltage by the output current, written as:

$$\frac{V_{out}^2}{R_{LOAD}} = \frac{\left(\frac{4 \cdot n \cdot V_{out}}{\sqrt{2}\pi}\right)^2}{R_{ac}}$$

Re-arranging the formula gives the equivalent AC resistor:

$$R_{ac} = \frac{8 \cdot n^2}{\pi^2} R_{LOAD}$$

The transfer ratio of the equivalent circuit can be obtained as following:

$$M = \left| \frac{\frac{j \cdot \omega \cdot L_m \cdot R_{ac}}{j \cdot \omega \cdot L_m + R_{ac}}}{j \cdot \omega \cdot L_r + \frac{1}{j \cdot \omega \cdot C_r} + \frac{j \cdot \omega \cdot L_m \cdot R_{ac}}{j \cdot \omega \cdot L_m + R_{ac}}} \right|$$

Simplifying to:

$$M = \left| \frac{1}{1 + \frac{L_r}{L_m} - \frac{1}{\omega^2 \cdot L_m \cdot C_r} + \frac{j \omega \cdot L_r}{R_{ac}} - \frac{j}{\omega \cdot C_r \cdot R_{ac}}} \right|$$

With the following definitions, calculation of M can be further simplified:

$$F_{r1} = \frac{1}{2\pi\sqrt{L_r \cdot C_r}}, \quad x = \frac{F_{sw}}{F_{r1}}, \quad \omega = 2\pi F_{sw} = 2\pi \cdot x \cdot F_{r1} = \frac{x}{\sqrt{L_r \cdot C_r}},$$

$$k = \frac{L_m}{L_r}, \quad R_{ac} = \frac{8 \cdot n^2 \cdot R_{LOAD}}{\pi^2}, \quad Q = \frac{2\pi F_{r1} \cdot L_r}{R_{ac}} = \frac{1}{2\pi F_{r1} \cdot C_r \cdot R_{ac}}$$

$$M = \left| \frac{1}{1 + \frac{1}{k} \cdot \left(1 - \frac{1}{x^2}\right) + j \cdot Q \cdot \left(x - \frac{1}{x}\right)} \right|$$

Or,

$$M = \frac{1}{\sqrt{\left[1 + \frac{1}{k} \cdot \left(1 - \frac{1}{x^2}\right)\right]^2 + \left[Q \cdot \left(x - \frac{1}{x}\right)\right]^2}}$$

Per Figure 15, M is also equal to the output voltage to bus voltage ratio:

$$M = \frac{n \cdot V_{out} \cdot \frac{4}{\pi}}{2 \cdot \frac{V_{bus}}{\pi}} = \frac{V_{out}}{V_{bus}} \cdot 2 \cdot n$$

So the conversion ratio of output voltage V_{out} to bus voltage V_{bus} is:

$$\frac{V_{out}}{V_{bus}} = \frac{M}{2 \cdot n}$$

4. Transformer and Resonant Circuit Design

The system input data:

| Parameter | Unit | Description | Value |
|-----------------|------|---------------------------------|----------|
| $V_{bus_{max}}$ | V | The maximum DC bus voltage | 480 |
| $V_{bus_{min}}$ | V | The minimum DC bus voltage | 440 |
| $V_{bus_{nom}}$ | V | The nominal DC bus voltage | 460 |
| V_{out} | V | The DC output voltage | 48 |
| I_{out} | A | The output load current | 1.4 |
| F_{r1} | kHz | The resonant frequency | 60 |
| F_{max} | kHz | The maximum switching frequency | 120 |
| D_{max} | | The maximum duty-cycle | 0.5 |
| | | | |
| | | | |
| | | Transformer core size | E32/16/9 |

Note: Typically $F_{max} < 2 \times F_{r1}$ because the parasitic capacitance in the system introduces a third resonant frequency that could cause the output voltage to increase with switching frequency at no load if the maximum switching frequency is higher than the limit.

Step 1: Calculate the transformer turns ratio

$$n = \frac{V_{bus(max)}}{2 \cdot V_{out}},$$

$$n = \frac{480}{2 \cdot 48} = 5$$

The transformer turns ratio is calculated with the maximum input voltage to make sure the output is always under regulation, including the worst case high-line voltage and no load condition.

Step 2: Choose k value

k is the ratio between the transformer magnetizing inductance and the resonant inductance. Smaller k value gives steeper gain curve, especially at the below resonant ZVS region as shown in figure 16. The output voltage is more sensitive to frequency variation with smaller k factor.

 


Figure16: k factor

A higher k value results in higher magnetizing inductance and thus lower magnetizing current in the transformer primary winding resulting in lower circulating power losses. However higher magnetic inductance could also cause non-ZVS switching at high line and zero load condition where the circulating current is too small to fully charge / discharge the VS node during dead-time.

The recommended range of k is from 3 to 10. In this case $k = 7$ is chosen.

Step 3: Calculate Qmax to maintain ZVS operation at the maximum load under the minimum input voltage

The input impedance of the equivalent resonant circuit (Figure 15) is given by:

$$Z_{in} = j \cdot \omega \cdot L_r + \frac{1}{j \cdot \omega \cdot C_r} + \frac{j \cdot \omega \cdot L_m \cdot R_{ac}}{j \cdot \omega \cdot L_m + R_{ac}}$$

$$Z_{in} = Q \cdot R_{ac} \left| \frac{k^2 \cdot x^2 \cdot Q}{1 + k^2 \cdot x^2 \cdot Q^2} + j \left(x - \frac{1}{x} + \frac{x \cdot k}{1 + k^2 \cdot x^2 \cdot Q^2} \right) \right|$$

To keep the converter working in soft switching mode the operating point should remain in the ZVS region as shown in figure 10. The ZVS-ZCS boundary line is defined by the phase angle of Z_{in} $\Phi(Z_{in})=0$ (the boundary condition between capacitive and inductive load), i.e. the imaginary part of Z_{in} is zero. With this condition we can calculate the maximum Q which allows the converter to stay in ZVS. The maximum Q happens at the minimum input voltage and the maximum load.

$$Q_{max} = \frac{1}{k} \cdot \frac{\sqrt{1 + k \cdot \left(1 - \frac{1}{M_{max}^2}\right)}}{M_{max}^2 - 1} = \frac{1}{k} \cdot \frac{\sqrt{1 + k \cdot \left[1 - \frac{1}{\left(2 \cdot n \cdot \frac{V_{out}}{V_{inmin}}\right)^2}\right]}}{\left(2 \cdot n \cdot \frac{V_{out}}{V_{inmin}}\right)^2 - 1}$$

Where M_{max} is the maximum conversion ratio at the minimum input voltage,

$$Q_{max} = 0.523$$

Step 4: Calculate the minimum switching frequency

The minimum switching frequency occurs at the maximum load and minimum input voltage with the previous calculated maximum Q_{max} . As Q_{max} is defined by $\text{Im}(Z_{in})=0$,

$$\left(x - \frac{1}{x} + \frac{x \cdot k}{1 + k^2 \cdot x^2 \cdot Q_{max}^2}\right) = 0$$

The F_{min} can be calculated with:

$$x_{min} = \frac{1}{\sqrt{1 + k \cdot \left(1 - \frac{1}{M_{max}^2}\right)}} = \frac{1}{\sqrt{1 + k \cdot \left[1 - \frac{1}{\left(\frac{2n \cdot V_{out}}{V_{inmin}}\right)^2}\right]}}$$

$$x_{min} = 0.736$$

$$F_{min} = x_{min} \cdot F_{r1} = 44.2 \text{ KHz}$$

Step 5: Calculate L_r , C_r and L_m

As Q_{max} happens at the maximum load, so the resonant components L_r , C_r and L_m can be calculated per the Q_{max} value that had obtained in step 3:

$$R_{LOAD} = \frac{V_{out}}{I_{out}} = \frac{48V}{1.4A} = 34.3\Omega$$

$$R_{ac} = \frac{8 \cdot n^2 \cdot R_{LOAD}}{\pi^2} = \frac{8 \times 5^2 \times 34.5}{\pi^2} = 699\Omega$$

$$L_r = \frac{Q_{max} \cdot R_{ac}}{2 \cdot \pi \cdot F_{r1}} = \frac{0.523 \times 699}{2 \cdot \pi \cdot 44.2 \cdot 10^3} = 1.32mH$$

$$C_r = \frac{1}{2 \cdot \pi \cdot F_{r1} \cdot Q_{max} \cdot R_{ac}} = \frac{1}{2 \cdot \pi \cdot 44.2 \cdot 10^3 \times 0.523 \times 699} = 9.85nF$$

Choose the nearest standard capacitor value for C_r , $C_r = 10nF$

Recalculate F_{r1} to keep the same Q_{max} with the selected C_r capacitor:

$$F_{r1} = \frac{1}{2 \cdot \pi \cdot C_r \cdot Q_{max} \cdot R_{ac}} = 43.5kHz$$

Recalculate L_r with the selected C_r and F_{r1} :

$$L_r = \frac{Q_{max} \cdot R_{ac}}{2 \cdot \pi \cdot F_{r1}} = 1.33mH$$

The actual L_r value should be lower than the calculated value to stay in ZVS region.

Now calculate L_m value based on L_r and the k factor that preset in step 2:

$$L_m = L_r \cdot k = 1.33 \times 7 = 9.31mH$$

Step 6: Calculate transformer primary and secondary turns

The standard half-bridge equation for the transformer turns number calculation is used here:

$$N_p = \frac{V_{in \min} \cdot D_{\max}}{2 \cdot \Delta B \cdot A_e \cdot F_{\min}}$$

With $\Delta B = 0.2T$, $A_e = 0.83cm^2$ (ETD49), $F_{\min} = 28kHz$, $V_{in \min} = 440V$, $D_{\max} = 0.5$

$$N_p = \frac{440 \times 0.5}{2 \times 0.2 \times 0.83 \times 28} \times 10 = 235$$

$$N_s = \frac{N_p}{n} = \frac{235}{5} = 47$$

The transformer was designed to be capable of operating down to 28kHz to provide a safety margin although the minimum frequency is 43.5kHz in this design. N_p was rounded to the nearest number divisible by n so that N_s would come out as a whole number.

Step 7: Calculate transformer primary and secondary current

In most LLC converter designs the minimum switching frequency is set below the resonant frequency F_{r1} in order to maintain output voltage regulation at low line and full load. When the switching frequency is lower than the resonant frequency F_{r1} , the current waveform is shown as in figure 17.

 


Figure17: Transformer primary current at full load and minimum input voltage

I_1 is the current where the resonant current in L_r equals the magnetizing current in L_m . This is also the point where C_r and L_r cease to resonate for the first half-period of F_{r1} . At this point, no more energy is delivered to the load and the output diodes are not conducting. C_r starts to resonate with $L_r + L_m$ until the switching MOSFETs changes state. I_1 can be calculated as:

$$I_1 = \frac{n \cdot V_{out}}{2 \cdot L_m \cdot 2 \cdot F_{r1}} = 0.15A$$

The peak and RMS value of primary current can be estimated as:

$$I_{pri(pk)} = \sqrt{\left(\frac{I_{out} \cdot \pi}{2 \cdot n}\right)^2 + I_1^2} = 0.47A$$

$$I_{priRMS} = \frac{I_{pri(pk)}}{\sqrt{2}} = 0.33A$$

The RMS current is calculated by assuming a purely sinusoidal current waveform. The actual primary RMS current is therefore higher than the calculated value.

The current in each secondary winding is very close to a half-sinusoid, thus the peak and RMS current can be estimated by:

$$I_{spk} = \frac{I_{out} \cdot \pi}{2} = 2.2A$$

$$I_{srms} = \frac{I_{out} \cdot \pi}{4} = 1.1A$$

The wire gauge of primary and secondary windings should be selected according to the calculated RMS current.

Step 8: Calculate resonant capacitor voltage

The C_r waveform is shown as in Figure 18:

 


Figure 18: Typical resonant tank voltage and current waveforms

I_{L_m} is the transformer primary magnetizing current, not including the current delivered to the secondary load through an ideal transformer in parallel with L_m . The difference between I_{L_r} and I_{L_m} is the output current.

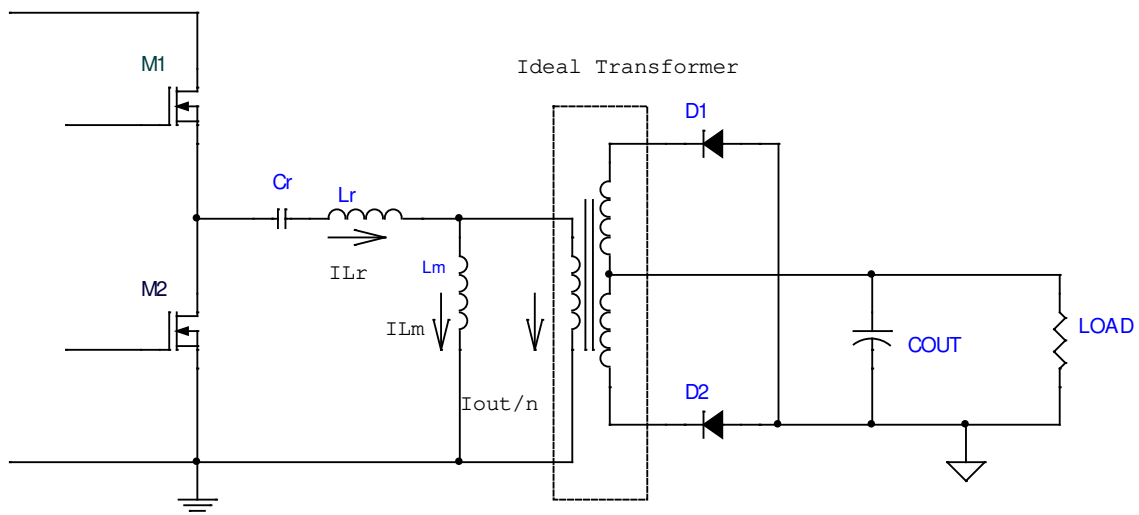


Figure 19: L_m and ideal transformer

The VC_r voltage reaches its peak when L_r current is crossing zero and it is at the mid-point of the input voltage when L_r current reaches its peak. The C_r voltage is at the maximum value when the VS node is at zero and is at the minimum value when the VS node is equal to V_{in} . VC_{rmin} and VC_{rmax} can be calculated as:

$$VC_{rmax} = n \cdot V_{out} + I_{pri(pk)} \times \sqrt{\frac{L_r}{C_r}}$$

$$VC_{rmin} = V_{in} - n \cdot V_{out} - I_{pri(pk)} \times \sqrt{\frac{L_r}{C_r}}$$

The peak to peak voltage ripple of VC_r is $VC_{rmax} - VC_{rmin}$:

$$VC_{rpk_pk} = 2n \cdot V_{out} + 2 \cdot I_{pri(pk)} \times \sqrt{\frac{L_r}{C_r}} - V_{in}$$

It can be seen that the maximum peak-to-peak voltage occurs at the maximum load and the minimum DC input V_{inmin} , the switching frequency is at the minimum F_{min} .

In this example:

$$V_{crpk_pk} = 2 \times 5 \times 48V + 2 \times 0.47A \times \sqrt{\frac{1.33mH}{10nF}} - 460V = 363V$$

The resonant capacitor C_r should be selected according to the capacitance value together with its voltage and current rating. A Polypropylene film capacitor should be used for minimum lower power loss. Polypropylene film capacitors are rated at DC voltage or 50Hz AC voltage with voltage de-rating at high frequency. The ability to withstand high frequency voltages is limited by thermal losses (power dissipation) and peak current capability. Even though the calculation result shows the maximum AC RMS voltage is 363V, a capacitor with higher voltage rating should be selected according to its frequency curve. Below is an example of EPCOS MKP capacitor B32612 (1000Vdc/250Vac).



 


Figure 20: V_{rms} vs. frequency curve of MKP capacitor B32612 @ $T_a \leq 90^\circ\text{C}$


In practice the transformer (T1) used on the IRPLLED5 board has a magnetizing inductance of 12mH and the series resonant inductor (L5) has a value of 1.5mH. This allows a low cost off the shelf inductor to be used for L5 while maintaining a similar ratio between L_m and L_r .

5. IRPPLLED5 Board Schematics

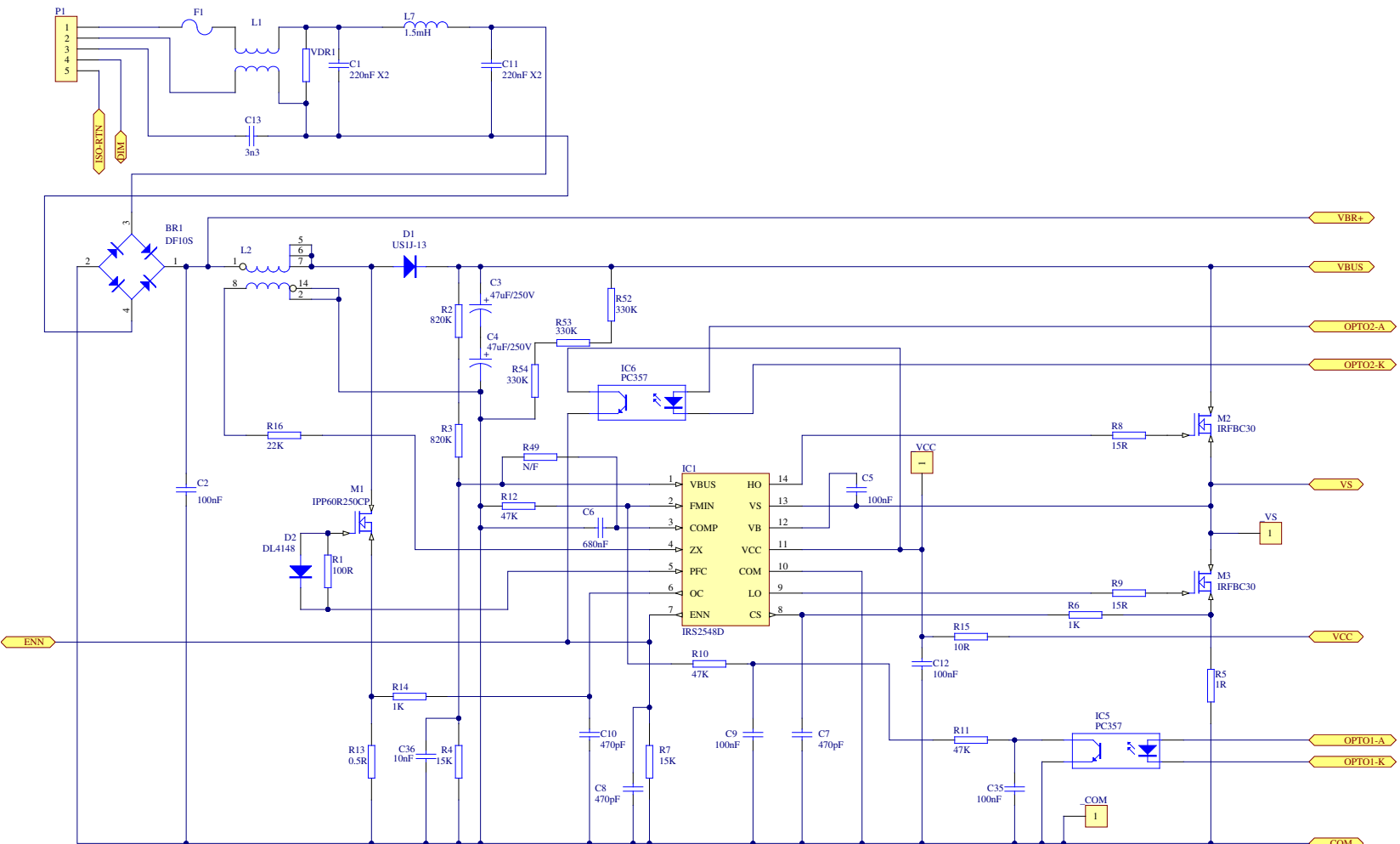

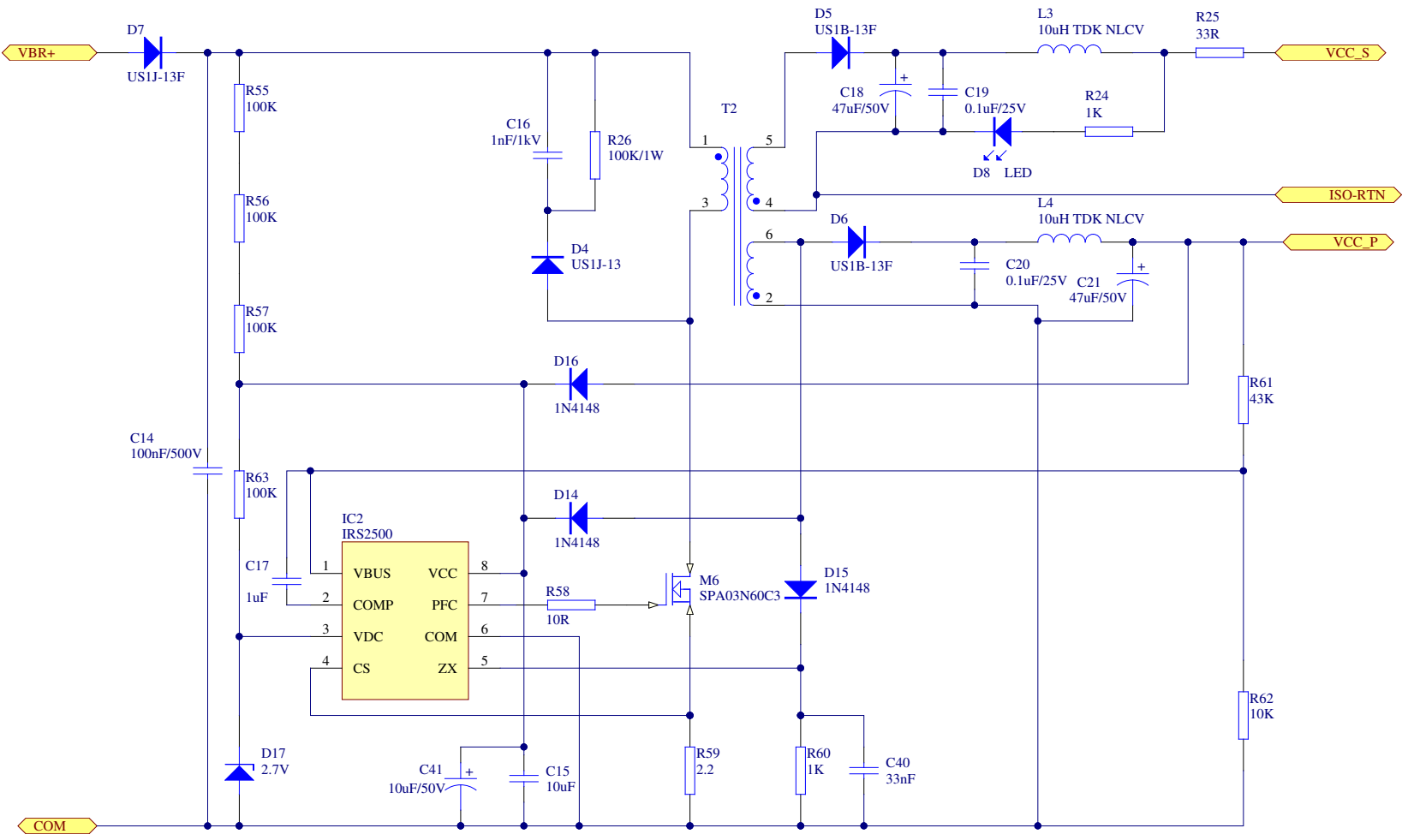

APPLICATION NOTE

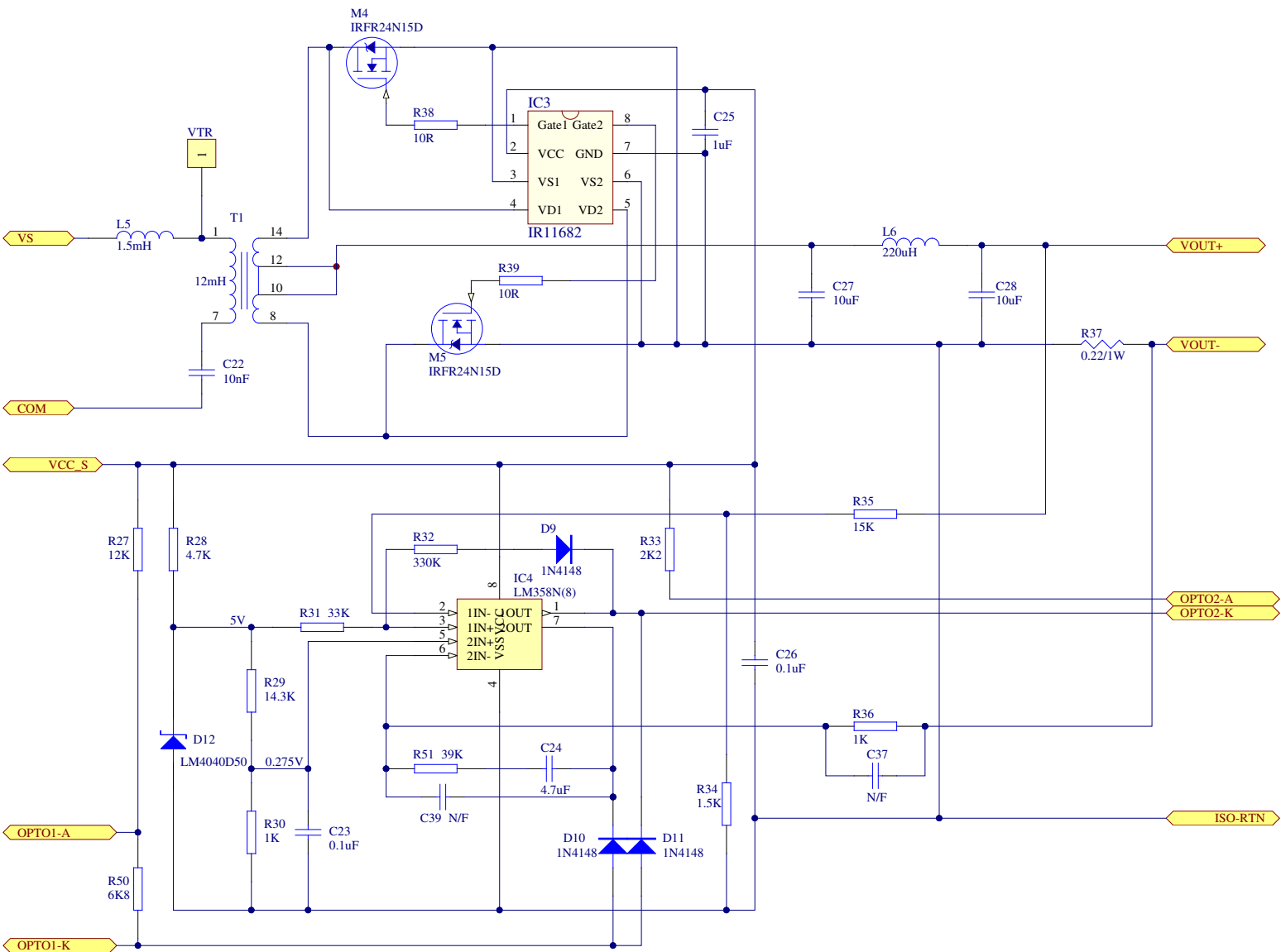

APPLICATION NOTE