

Chipsmall Limited consists of a professional team with an average of over 10 year of expertise in the distribution of electronic components. Based in Hongkong, we have already established firm and mutual-benefit business relationships with customers from, Europe, America and south Asia, supplying obsolete and hard-to-find components to meet their specific needs.

With the principle of "Quality Parts, Customers Priority, Honest Operation, and Considerate Service", our business mainly focus on the distribution of electronic components. Line cards we deal with include Microchip, ALPS, ROHM, Xilinx, Pulse, ON, Everlight and Freescale. Main products comprise IC, Modules, Potentiometer, IC Socket, Relay, Connector. Our parts cover such applications as commercial, industrial, and automotives areas.

We are looking forward to setting up business relationship with you and hope to provide you with the best service and solution. Let us make a better world for our industry!



Contact us

Tel: +86-755-8981 8866 Fax: +86-755-8427 6832

Email & Skype: info@chipsmall.com Web: www.chipsmall.com

Address: A1208, Overseas Decoration Building, #122 Zhenhua RD., Futian, Shenzhen, China









PORTNOTE®

Negative Battery Voltage SLIC Protection GR-1089-CORE Intra-building Solution

Solution Products



TBU-PL060-200-WH



Objective

The SLIC (Subscriber Line Interface Circuit) provides all the BORSCHT functions such as battery, ringing, supervision between the codec and telephone hand set. This PortNote® solution protects negative battery voltage solutions against surge and power contact threats.

Solution

1 TBU° High-Speed Protector: TBU-PL060-200-WH 2 MOV Devices: MOV-10D201K

Compliance

GR-1089-CORE intra-building, issue 5, port type 4.

- 120 V_{rms}, 25 A, 900 seconds withstand.
- \bullet 130 V_{rms} maximum AC withstand.
- \bullet Increased surge level to 5 kV, 500 A 2/10 $\mu s.$


Alternate Recommendations

Other PortNote® Solutions:

- SLIC Protection GR-1089-CORE Intra-building Solution
- Negative Battery Voltage SLIC Protection ITU-T Solution
- Dual Supply Voltage SLIC Protection ITU-T Solution

Benefit

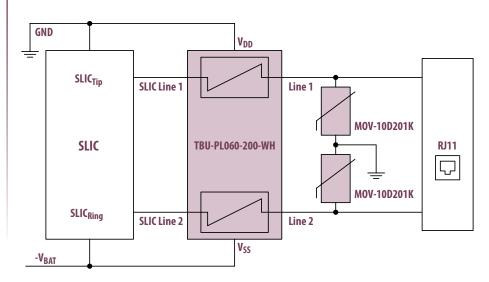This solution provides a high level of protection in a small PCB area.



The schematic above illustrates the application protection and does not constitute the complete circuit design. Customers should verify actual device performance in their specific applications.

Design Kit



PN-DESIGNKIT-20

BOURNS®

Fax + 41 - (0)417685510

Europe: *Tel* +41-(0)41 768 55 55 **A**

Americas: *Tel* +1-951 781-5500 *Fax* +1-951 781-5700

Asia-Pacific: *Tel* +886-2 256 241 17

Fax +886-2 256 241 16

Bourns* PortNote* solutions provide protection recommendations for typical port threats.

For more information, go to:

www.bourns.com

or email: protection@bourns.com

COPYRIGHT© 2012 • BOURNS, INC. • 6/12 • e/CPK1130 • "PortNote" is a registered service mark of Bourns, Inc. "Bourns" and "TBU" are registered trademarks of Bourns, Inc. in the U.S. and other countries.