



Chipsmall Limited consists of a professional team with an average of over 10 year of expertise in the distribution of electronic components. Based in Hongkong, we have already established firm and mutual-benefit business relationships with customers from,Europe,America and south Asia,supplying obsolete and hard-to-find components to meet their specific needs.

With the principle of “Quality Parts,Customers Priority,Honest Operation,and Considerate Service”,our business mainly focus on the distribution of electronic components. Line cards we deal with include Microchip,ALPS,ROHM,Xilinx,Pulse,ON,Everlight and Freescale. Main products comprise IC,Modules,Potentiometer,IC Socket,Relay,Connector.Our parts cover such applications as commercial,industrial, and automotives areas.

We are looking forward to setting up business relationship with you and hope to provide you with the best service and solution. Let us make a better world for our industry!



Contact us

Tel: +86-755-8981 8866 Fax: +86-755-8427 6832

Email & Skype: info@chipsmall.com Web: www.chipsmall.com

Address: A1208, Overseas Decoration Building, #122 Zhenhua RD., Futian, Shenzhen, China



CAN-bus Surge Protection

Solution Products



TBU-CA065-100-WH



MOV-10D201K



CDSOT23-T12LC

Design Kit



PN-DESIGNKIT-26

Objective

CAN is a serial bus with a message-based protocol designed specifically for automotive applications but can also be used in other areas such as industrial automation and medical equipment. Bit rates up to 1 Mbit/s are possible at network lengths below 40 m. This solution provides protection from high energy surges originating from switching and/or higher voltage transients.

Solution

- 2 TBU® High-Speed Protectors:
TBU-CA065-100-WH
- 2 MOVs: MOV-10D201K
- 2 TVS Diode Arrays: CDSOT23-T12LC

Compliance


- IEC 61000-4-4 EFT
- IEC 61000-4-5 Surge / Lightning

Alternate Recommendations

- 2x CDSOT23-S2004

Benefit

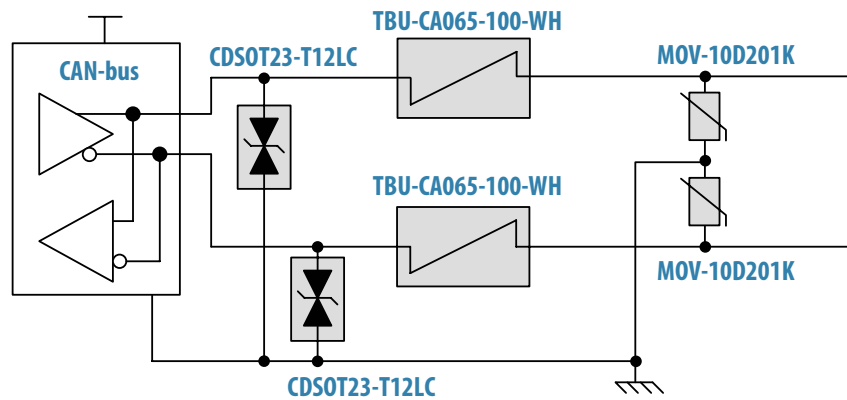This solution is designed to protect the interface from surge events.



The schematic above illustrates the application protection and does not constitute the complete circuit design. Customers should verify actual device performance in their specific applications.