



Chipsmall Limited consists of a professional team with an average of over 10 year of expertise in the distribution of electronic components. Based in Hongkong, we have already established firm and mutual-benefit business relationships with customers from,Europe,America and south Asia,supplying obsolete and hard-to-find components to meet their specific needs.

With the principle of "Quality Parts,Customers Priority,Honest Operation,and Considerate Service",our business mainly focus on the distribution of electronic components. Line cards we deal with include Microchip,ALPS,ROHM,Xilinx,Pulse,ON,Everlight and Freescale. Main products comprise IC,Modules,Potentiometer,IC Socket,Relay,Connector.Our parts cover such applications as commercial,industrial, and automotives areas.

We are looking forward to setting up business relationship with you and hope to provide you with the best service and solution. Let us make a better world for our industry!



Contact us

Tel: +86-755-8981 8866 Fax: +86-755-8427 6832

Email & Skype: info@chipsmall.com Web: www.chipsmall.com

Address: A1208, Overseas Decoration Building, #122 Zhenhua RD., Futian, Shenzhen, China



LTC6268 and LTC6268-10 3-Channel SOT-23 Transimpedance Amplifier

DESCRIPTION

Demonstration Circuit 2414A has layouts for three channels of SOT-23 transimpedance amplifiers. Each of the three layouts applies different techniques achieving various parasitic feedback capacitances (C_F). The upper channel, U3, assumes a low Transimpedance gain, has a parasitic C_F of 0.1pF, and provides a footprint for an additional component C_F in an 0402 footprint (C29). The lower channel, U1, assumes high transimpedance gain and was laid out to minimize C_F , achieving approximately 7fF, although the real situation is more complex. The middle channel, U2, assumes a middle case. The outputs of the circuit are laid out for SMA edge connectors. The inputs consist of six pads per channel along the edge where a through-hole photodiode can be mounted, with provision

for any photodiode pinout. The reverse bias voltage for the photodiode can be applied at a V_{BB} turret, or can be taken from V^+ or V^- through jumper JP4. The V_{BB} traces were spaced according to IPC2221 for 150V working voltage, so high voltage APDs can be applied. **Take caution when working with high voltages to avoid contact with any part of the VBB trace.** Because of the many possible varieties of population, the board is stocked as a bare unpopulated board.

Design files for this circuit board are available at <http://www.linear.com/demo/DC2414A>

LT, LT, LTC, LTM, Linear Technology and the Linear logo are registered trademarks of Linear Technology Corporation. All other trademarks are the property of their respective owners.

BOARD PHOTO

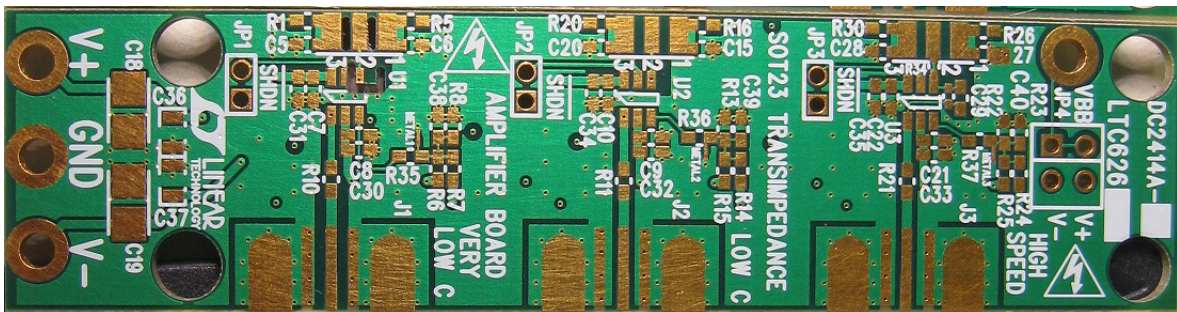


Figure 1. Topside Bare PCB DC2414A, for SOT-23 LTC®6268 and LTC6268-10 Op Amps

OPERATING PRINCIPLES

The **LTC6268** and **LTC6268-10** have gain bandwidth products of 500MHz and 4GHz respectively. At low transimpedance gain with small photodiodes (say 10k gain and 1pF photodiode) the bandwidth achieved can be quite high, such as 200MHz. The upper channel, U3, is best suited for these types of applications. The parasitic C_F around the R_F is about 0.1pF in this channel, and an 0402 footprint is provided so additional C_F can be added. The R_F and C_F in this highest speed channel are on the topside to avoid vias, and are close to the op amp.

At very high gains, much less bandwidth is achievable both because the gain is high and because parasitic feedback capacitance reduces the effective impedance of the feedback resistor prematurely. For both the low capacitance channels, the R_F is mounted on the bottom side for the most effective shielding from the output trace.

But the resistor and its pads also have parasitic capacitance. For example, a typical 0805 resistor has about 70fF of capacitance in air, so a 10M resistor would already be 3dB lower impedance at 220kHz. However, the circuit is not “in air,” but on a board; and by placing some grounded copper underneath a resistor, the parasitic C_F can be greatly reduced.

The middle channel, U2, applies this technique rather modestly under an 0603 resistor, while the lower channel, U1, has a rather extreme layout under a 1206 resistor. These channels have parasitic C_F of about 33fF and “7fF,” respectively, with a regular Vishay CRCW resistor installed. However, the “7fF” is a simplification, derived from the fact that at 10M of gain, that channel achieves rise times as low as 100ns. In fact, however, the extended body of the resistor and the ground underneath it cause some capacitive loading of the resistor element, perhaps best modelled as an RC network as shown in Figure 2.

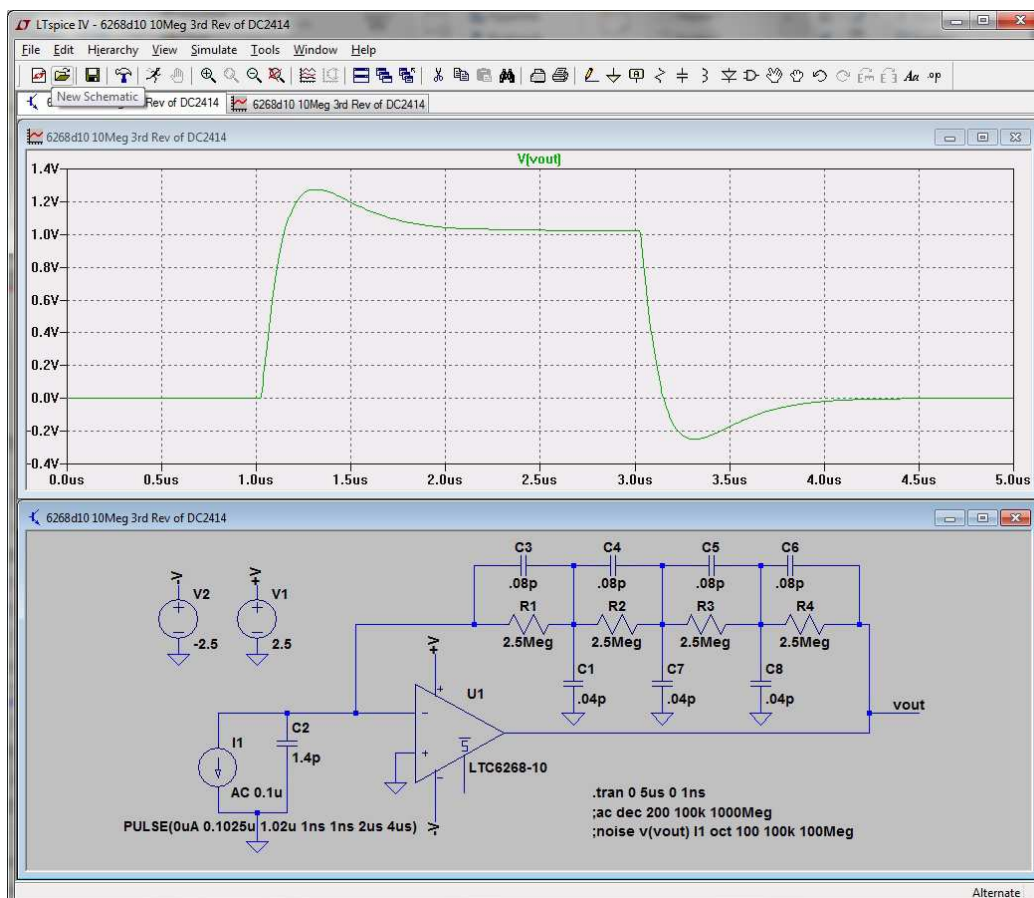


Figure 2. Capacitively Loaded Resistor Element Approximation for the U1 Channel, with $R_F = 10M$

OPERATING PRINCIPLES

Split Supply vs Single Supply

The default configuration of the board assumes a $\pm 1.55\text{V}$ to $\pm 2.5\text{V}$ split supply. To use a single supply, short V^- to ground at the GND and V^- turrets. Also, in order to keep inductance low at the op amp's V^- connection, short the V^- bypass capacitor locations near the op amp (C8/C9/C21) depending on which op amp is installed. Valid single supplies are 3.1V to 5V. When using a single supply, you will probably want to change the default voltage on the +input.

The +Input

On all 3 channels, the +input is grounded through R35/R36/R37 and a trace called "METAL" to ground. The series resistor may be a 0Ω jumper, or a 33Ω to 100Ω resistor to de-Q the path. To create a voltage other than ground at the +input, cut the "METAL" trace and create the desired voltage with the resistor strings there (R6-8, R13-15, and R23-25). Capacitors C38/C39/C40 are provided to filter the resistor noise and any supply ripple.

V_{BB}

The photodiode reverse bias can be applied at the V_{BB} turret. (Note that all "turrets" are close to the edges of the board, so clips can be applied directly to the plated holes, thus not requiring turrets to be populated.) V_{BB} can also be taken from V^+ or V^- though jumper selection JP4. **If V_{BB} will be a high voltage, be careful not to touch it when energized, as the trace runs along the entire edge of the photodiode side of the board. Lightning bolts are placed in the silkscreen as a reminder when high voltage is used for V_{BB} .** Various pads are provided to RC connect V_{BB} to the cathode or anode of the photodiode. In practice, very few of the passives shown around the photodiode will be installed. Which ones will be installed will depend on the photodiode pinout and whether the TIA will be anode or cathode connected.

Shutdown (Floats "On")

The LTC6268 _SHDN pin floats high, turning the op amp on. If you want to play with the shutdown function, install JP1/JP2/JP3. Placing the shunt on the jumper pulls the _SHDN to ground turning off the op amp.

PCB Material

The PCB dielectric, chosen for its low dielectric constant of 3.4, is Nelco-4000-EP-SI. If FR-4 is used with a similar layout, remember that the parasitic capacitances will increase by 30% to 40%. Note that this demo board is not fabricated to controlled impedance. The special material was chosen purely for low capacitance.

Checking for High Frequency Oscillations in LTC6268-10 Designs

The LTC6268-10 has a gain bandwidth product of 4GHz. When checking an LTC6268-10 design for any problems, it is best to use an oscilloscope with adequate bandwidth ($>1\text{GHz}$), so that any high frequency oscillations are not hidden by limited scope bandwidth. If using a spectrum analyzer, it should have at least 3GHz of bandwidth.

The DC2414A high speed channel was designed with little ground copper in the photodiode region, to support the lowest input capacitance possible. However, when the photodiode is larger, then input inductance can become an issue. For example, at 12pF of lumped element photodiode C, and with the nominal $20\text{k} \parallel 0.1\text{pF}$ feedback network in place, $\sim 30\text{mV}_{\text{P-P}}$ oscillations were detected at 1.4GHz. Placing a grounded copper foil tape along the bottom side copper void thoroughly quenched the oscillations.

SAMPLE POPULATION


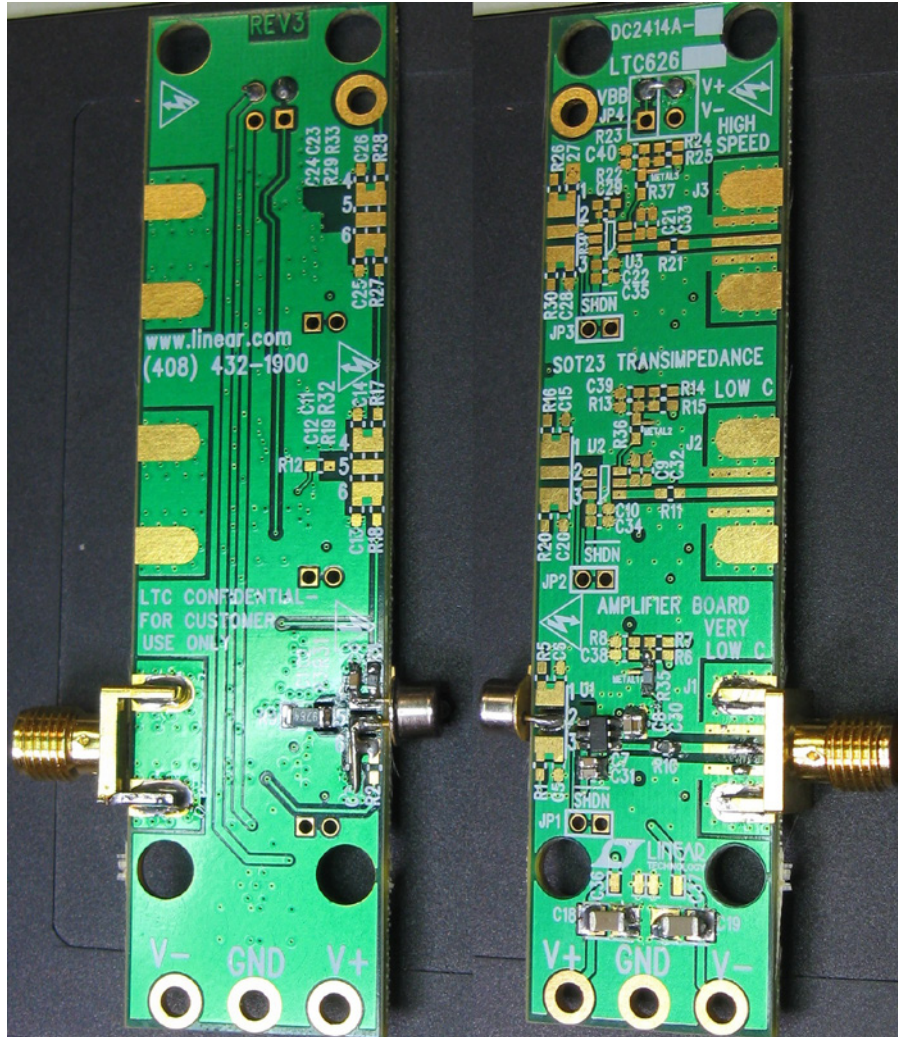


Figure 3. An Example of a Population of the Very Low Capacitance Channel Around U1. Photodiode is OSI FCI-125G-006HRL, Anode Connected to the TIA Input, so Cathode is Held High to V_{BB} Shorted to V^+ . R_F is 9.76M on the Bottom Side (Left)

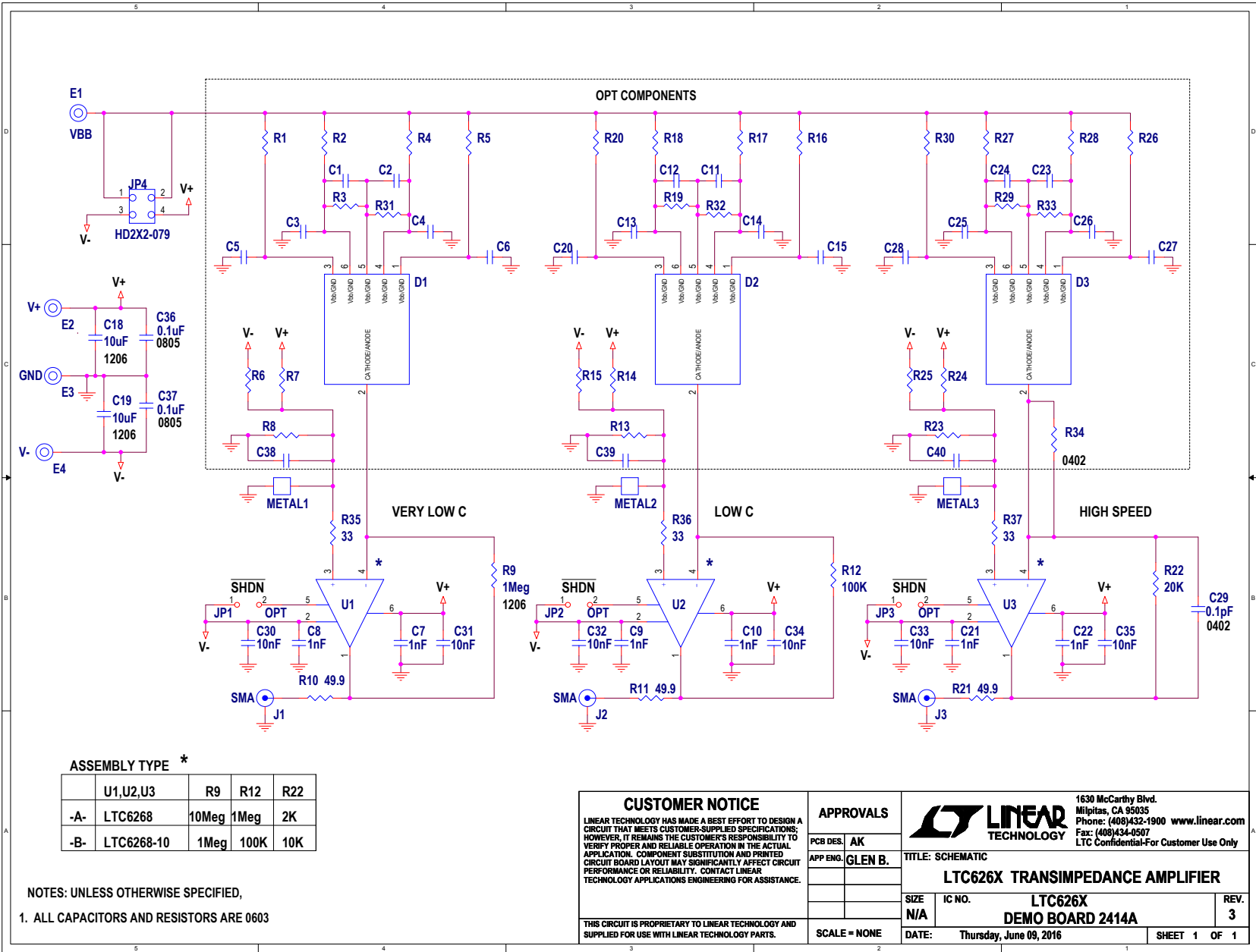

ASSEMBLY TYPE *

	U1,U2,U3	R9	R12	R22
-A-	LTC6268	10Meg	1Meg	2K
-B-	LTC6268-10	1Meg	100K	10K

NOTES: UNLESS OTHERWISE SPECIFIED,
1. ALL CAPACITORS AND RESISTORS ARE 0603

CUSTOMER NOTICE		APPROVALS		LINEAR TECHNOLOGY		
LINEAR TECHNOLOGY HAS MADE A BEST EFFORT TO DESIGN A CIRCUIT THAT MEETS CUSTOMER-SUPPLIED SPECIFICATIONS; HOWEVER, IT REMAINS THE CUSTOMER'S RESPONSIBILITY TO VERIFY PROPER AND RELIABLE OPERATION IN THE ACTUAL APPLICATION. COMPONENT SUBSTITUTION AND PRINTED CIRCUIT BOARD LAYOUT MAY SIGNIFICANTLY AFFECT CIRCUIT PERFORMANCE OR RELIABILITY. CONTACT LINEAR TECHNOLOGY APPLICATIONS ENGINEERING FOR ASSISTANCE.		PCB DES. AK	<p>1630 McCarthy Blvd. Milpitas, CA 95035 Phone: (408)432-1900 www.linear.com Fax: (408)434-0507 LTC Confidential-For Customer Use Only</p>			
		APP ENG. GLEN B.				
THIS CIRCUIT IS PROPRIETARY TO LINEAR TECHNOLOGY AND SUPPLIED FOR USE WITH LINEAR TECHNOLOGY PARTS.		SCALE = NONE	TITLE: SCHEMATIC LTC626X TRANSIMPEDANCE AMPLIFIER		REV. 3	
		DATE: Thursday, June 09, 2016	SIZE N/A	IC NO. LTC626X DEMO BOARD 2414A	SHEET 1 OF 1	

DEMO MANUAL DC2414A

DEMONSTRATION BOARD IMPORTANT NOTICE

Linear Technology Corporation (LTC) provides the enclosed product(s) under the following **AS IS** conditions:

This demonstration board (DEMO BOARD) kit being sold or provided by Linear Technology is intended for use for **ENGINEERING DEVELOPMENT OR EVALUATION PURPOSES ONLY** and is not provided by LTC for commercial use. As such, the DEMO BOARD herein may not be complete in terms of required design-, marketing-, and/or manufacturing-related protective considerations, including but not limited to product safety measures typically found in finished commercial goods. As a prototype, this product does not fall within the scope of the European Union directive on electromagnetic compatibility and therefore may or may not meet the technical requirements of the directive, or other regulations.

If this evaluation kit does not meet the specifications recited in the DEMO BOARD manual the kit may be returned within 30 days from the date of delivery for a full refund. **THE FOREGOING WARRANTY IS THE EXCLUSIVE WARRANTY MADE BY THE SELLER TO BUYER AND IS IN LIEU OF ALL OTHER WARRANTIES, EXPRESSED, IMPLIED, OR STATUTORY, INCLUDING ANY WARRANTY OF MERCHANTABILITY OR FITNESS FOR ANY PARTICULAR PURPOSE. EXCEPT TO THE EXTENT OF THIS INDEMNITY, NEITHER PARTY SHALL BE LIABLE TO THE OTHER FOR ANY INDIRECT, SPECIAL, INCIDENTAL, OR CONSEQUENTIAL DAMAGES.**

The user assumes all responsibility and liability for proper and safe handling of the goods. Further, the user releases LTC from all claims arising from the handling or use of the goods. Due to the open construction of the product, it is the user's responsibility to take any and all appropriate precautions with regard to electrostatic discharge. Also be aware that the products herein may not be regulatory compliant or agency certified (FCC, UL, CE, etc.).

No License is granted under any patent right or other intellectual property whatsoever. **LTC assumes no liability for applications assistance, customer product design, software performance, or infringement of patents or any other intellectual property rights of any kind.**

LTC currently services a variety of customers for products around the world, and therefore this transaction **is not exclusive**.

Please read the DEMO BOARD manual prior to handling the product. Persons handling this product must have electronics training and observe good laboratory practice standards. **Common sense is encouraged.**

This notice contains important safety information about temperatures and voltages. For further safety concerns, please contact a LTC application engineer.

Mailing Address:

Linear Technology
1630 McCarthy Blvd.
Milpitas, CA 95035

Copyright © 2004, Linear Technology Corporation