# imall

Chipsmall Limited consists of a professional team with an average of over 10 year of expertise in the distribution of electronic components. Based in Hongkong, we have already established firm and mutual-benefit business relationships with customers from, Europe, America and south Asia, supplying obsolete and hard-to-find components to meet their specific needs.

With the principle of "Quality Parts, Customers Priority, Honest Operation, and Considerate Service", our business mainly focus on the distribution of electronic components. Line cards we deal with include Microchip, ALPS, ROHM, Xilinx, Pulse, ON, Everlight and Freescale. Main products comprise IC, Modules, Potentiometer, IC Socket, Relay, Connector. Our parts cover such applications as commercial, industrial, and automotives areas.

We are looking forward to setting up business relationship with you and hope to provide you with the best service and solution. Let us make a better world for our industry!



# Contact us

Tel: +86-755-8981 8866 Fax: +86-755-8427 6832 Email & Skype: info@chipsmall.com Web: www.chipsmall.com Address: A1208, Overseas Decoration Building, #122 Zhenhua RD., Futian, Shenzhen, China





#### **General Description**

The TH7108 antenna board is designed to optimally match the differential power amplifier output to a loop antenna. The TH7108 can be populated either for FSK, ASK or FM transmission. The default population is for FSK or ASK transmission. Adding a varactor diode can easily be done in order to modify the circuit for analog FM. The evaluation board contains a differential-drive loop antenna printed on the PCB (Printed Circuit Board). The size of the loop antenna is matched to the resonant frequency.

Board layout data in Gerber format is available on request.

#### Features

- □ Fully integrated, PLL-stabilized VCO
- Flexible frequency range from 850 MHz to 930 MHz
- FSK through crystal pulling allows modulation from DC to 20 kbit/s
- High deviation possible for wideband data transmission
- ASK achieved by on/off keying of internal power amplifier
- □ FM possible with external varactor
- □ Wide power supply range from 2.2 V to 5.5 V
- □ High over-all frequency accuracy
- Very low standby current

- Adjustable equivalent radiated power (ERP) range from -20 dBm to -6 dBm
- Adjustable current consumption from 6.2 mA to 12.5 mA
- Frequency deviation and center frequency independently adjustable
- Differential output well-suited for loop antenna
- External clock available for µC drive, down to 1.9 V supply
- Clock only mode
- □ Conforms to EN 300 220 standard

#### Ordering Information Part No.

EVB7108-868-FSK EVB7108-868-ASK EVB7108-915-FSK EVB7108-915-ASK

### Applications

- □ Keyless car and central locking
- □ Low-power telemetry
- Alarm and security systems

- General digital data transmission
- □ General analog audio signal transmission



## Theory of Operation

#### General

As depicted in Fig.1, the TH7108 transmitter consists of a fully integrated voltage-controlled oscillator (VCO), a divide-by-32 divider (div32), a phase-frequency detector (PFD) and a charge pump. An external loop filter at pin LF determines the dynamic behaviour of the PLL and suppresses reference spurious signals.

The VCO's output signal feeds the power amplifier (PA). RF signal power P<sub>o</sub> can be adjusted in six steps from P<sub>o</sub> = -15 dBm to +1 dBm either by changing the value of resistor R<sub>PS</sub> or by varying the voltage V<sub>PS</sub> at pin PS. The open-collector differential output (OUT1, OUT2) can be used to either directly drive a loop antenna or to be converted to a single-ended impedance by means of a balanced-to-unbalanced (balun) transformer. For maximum available output power, the differential output should be matched to a load of approx. 1 k $\Omega$ .

Bandgap biasing ensures stable operation of the IC at a power supply range of 2.2 V to 5.5 V.

#### **FSK Modulation**

A Colpitts crystal oscillator (XOSC) is used as the reference oscillator of a phase-locked loop (PLL) synthesizer. FSK modulation is achieved by pulling the crystal (XTAL) through the data. So a CMOS-compatible data stream applied at input DATA digitally modulates the XOSC. Two external pulling capacitors  $C_{X1}$  and  $C_{X2}$  allow the FSK deviation and center frequency to be adjusted independently. At DATA = LOW  $C_{X2}$  is connected in parallel to  $C_{X1}$  leading to the low-frequency component of the FSK spectrum ( $f_{min}$ ); while at DATA = HIGH  $C_{X2}$  is deactivated and the XOSC is set to its high frequency, leading to  $f_{max}$ .

An external reference signal can be directly ACcoupled to pin RO1. Then the TH7108 is used without an XTAL. The reference signal has to contain the FSK (or FM) and sets the carrier frequency.

#### Frequency Modulation (FM)

For FM operation an external varactor is required. It simply acts as a pulling capacitor connected in series to the crystal. Then the analog modulation signal, applied through a series resistor, directly modulates the XOSC.

#### **ASK Modulation**

The TH7108 can be ASK-modulated by applying data directly at pin PS. This turns the PA on and off and therefore leads to an ASK signal at the output.

#### Mode Control Logic

The mode control logic allows four different modes of operation as listed in the following table. The mode control pins ENCK and ENTX are pulleddown internally. This guarantees that the whole circuit is shut down if these pins are left floating. The clock output CKOUT can be used to drive a  $\mu$ C. This output can be activated by the ENCK pin as required for any specific application. Clock frequency is 1/8 of the reference crystal frequency. The clock output is slew-rate limited in order to keep spurious signal emission as low as possible. The voltage swing at CKOUT depends on the capacitive loading at this pin. It is approx. 2 V<sub>pp</sub> at C<sub>load</sub> = 5 pF.

ENCK	ENTX	Mode	Description			
0	0	all OFF	whole circuit in standby			
0	1	TX only	y TX functionality only, no clock available			
1	0	clock only	TX in standby and clock available			
1	1	all ON	TX functional and clock available			

Table 1: Modes of operation

For more detailed information, please refer to the latest TH7108 data sheet revision.



# Block Diagram


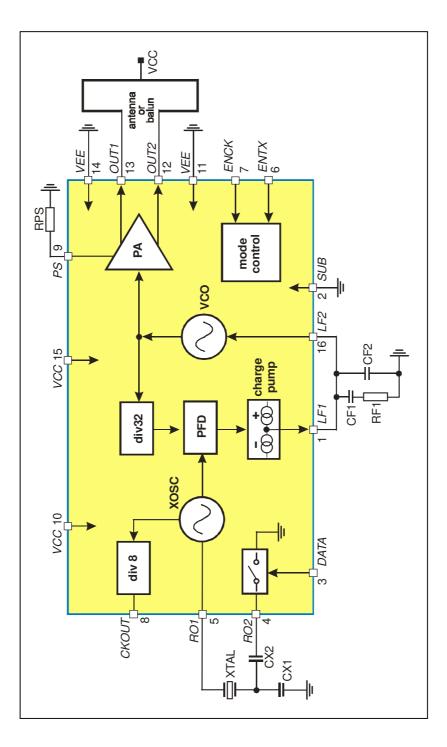


Fig. 1: TH7108 block diagram with external components

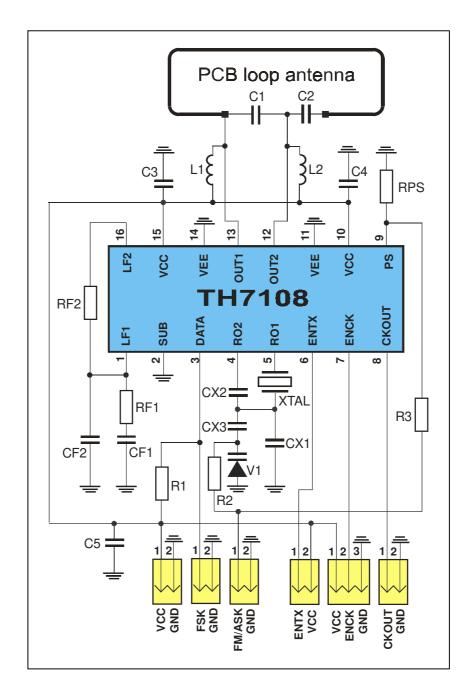


# Circuit Diagram





# PCB Top View

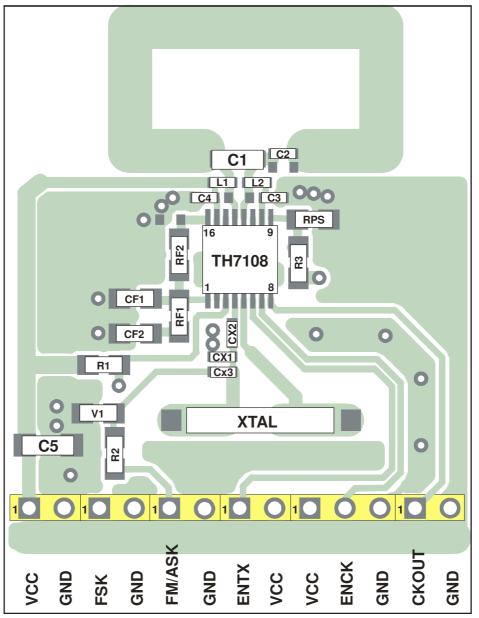

Board size is 34mm x 44mm

#### **Board Connection**

VCC	Power supply (2.2 V to 5.5 V)	ENCK	Mode control pin (see table 1)
FSK	Input for FSK data (CMOS)	ENTX	Mode control pin (see table 1)
FM/ASK	Input for FM signal (analog) or ASK data (CMOS)	GND	Several ground pins
CKOUT	Clock output (3.4 MHz)		



# **Board Component Values**

Part	Size	Value 868.3 MHz			Description		
CF1	0805	5.6 nF	4.7 nF	±10%	loop filter capacitor		
CF2	0805	27 pF	27 pF	±10%	loop filter capacitor		
CX1_ <sub>FSK</sub>	0603	56 pF	56 pF	±5%	XOSC capacitor for FSK ( $\Delta f = \pm 30 \text{ kHz}$ )		
CX1_ <sub>ASK</sub>	0603	18 pF	18 pF	±5%	XOSC capacitor for ASK, trimmed to $f_{C}$		
CX2	0603	1 nF	1 nF	±5%	XOSC capacitor, only needed for FSK		
CX3	0603	1 nF	1 nF	±10%	XOSC capacitor, only needed for FM		
C1	1206	2.2 pF	2.2 pF	±2%	antenna resonance capacitor		
C2	0805	1.2 pF	1 pF	±2%	antenna resonance capacitor		
C3	0603	330 pF	330 pF	±10%	blocking capacitor		
C4	0603	330 pF	330 pF	±10%	blocking capacitor		
C5	1206	220 nF	220 nF	±20%	blocking capacitor		
L1	0603	150 nH	150 nH	±10%	biasing inductor		
L2	0603	150 nH	150 nH	±10%	biasing inductor		
RF1	0805	1.6 kΩ	1.6 kΩ	±10%	loop filter resistor		
RF2	0805	2.0 kΩ	2.0 kΩ	±10%	loop filter resistor		
RPS	0805	47 kΩ	47 kΩ	±10%	power-select resistor		
R1	0805	470 kΩ	470 kΩ	±10%	optional pull-up resistor, typically not needed		
R2	0805	30 kΩ	30 kΩ	±10%	varactor bias resistor, only needed for FM		
R3	0805	0 Ω	0 Ω	±10%	ASK jumper, only needed for ASK		
V1	SOD323	BB535			varactor diode, only needed for FM		
XTAL	HC49/S	27.1344 MHz fundamental wave	28.5938 MHz fundamental wave	±30ppm calibration ±30ppm temp.	crystal, $C_{load}$ = 12 pF to 15 pF, $C_{0, max}$ = 7 pF, $R_{m, max}$ = 40 $\Omega$		
PCB loop antenna	long side length	18 mm	18 mm		on FR4 PCB material side length including length of C1 and C2		
PCB loop antenna	small side length	9 mm	9 mm		on FR4 PCB material		
PCB loop antenna	Line width	2 mm	2 mm		on FR4 PCB material		

The listed component values are default values. All values might be changed to fit to any specific application. As for example FSK deviation can be set by varying CX1 and CX2, output power at FSK/FM transmission can be changed through RPS or through RPS and R3 at ASK transmission, respectively.

Pads for C1 are for population of a fixed-value capacitor with size 1206 or a to use trimming capacitor either.



# Package Information

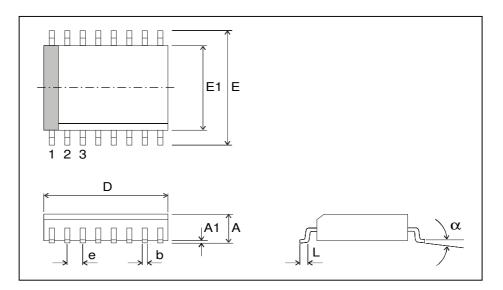


Fig. 2: QSOP16

all Dimension in mm, coplanarity < 0.1mm										
	D	E1	E	Α	A1	е	b	L	α	
min	4.80	3.81	5.79	1.35	0.10	0.635	0.20	0.40	0°	
max	4.98	3.99	6.20	1.75	0.25		0.30	1.27	8°	
all Dimension in inch, coplanarity < 0.004"										
min	0.189	0.150	0.228	0.0532	0.0040	0.025	0.008	0.016	0°	
max	0.196	0.157	0.244	0.0688	0.0098		0.012	0.050	8°	



### Disclaimer

Devices sold by Melexis are covered by the warranty and patent indemnification provisions appearing in its Term of Sale. Melexis makes no warranty, express, statutory, implied, or by description regarding the information set forth herein or regarding the freedom of the described devices from patent infringement. Melexis reserves the right to change specifications and prices at any time and without notice. Therefore, prior to designing this product into a system, it is necessary to check with Melexis for current information. This product is intended for use in normal commercial applications. Applications requiring extended temperature range, unusual environmental requirements, or high reliability applications, such as military, medical life-support or life-sustaining equipment are specifically not recommended without additional processing by Melexis for each application.

The information furnished by Melexis is believed to be correct and accurate. However, Melexis shall not be liable to recipient or any third party for any damages, including but not limited to personal injury, property damage, loss of profits, loss of use, interrupt of business or indirect, special incidental or consequential damages, of any kind, in connection with or arising out of the furnishing, performance or use of the technical data herein. No obligation or liability to recipient or any third party shall arise or flow out of Melexis' rendering of technical or other services.

© 2002 Melexis NV. All rights reserved.

For the latest version of this document. Go to our website at **www.melexis.com** 

Or for additional information contact Melexis Direct:

Europe and Japan: Phone: +32 1367 0495 E-mail: sales\_europe@melexis.com All other locations: Phone: +1 603 223 2362 E-mail: sales\_usa@melexis.com

QS9000, VDA6.1 and ISO14001 Certified