Ehipsmall

Chipsmall Limited consists of a professional team with an average of over 10 year of expertise in the distribution of electronic components. Based in Hongkong, we have already established firm and mutual-benefit business relationships with customers from,Europe,America and south Asia,supplying obsolete and hard-to-find components to meet their specific needs.

With the principle of "Quality Parts,Customers Priority,Honest Operation,and Considerate Service",our business mainly focus on the distribution of electronic components. Line cards we deal with include Microchip,ALPS,ROHM,Xilinx,Pulse,ON,Everlight and Freescale. Main products comprise IC,Modules,Potentiometer,IC Socket,Relay,Connector.Our parts cover such applications as commercial,industrial, and automotives areas.

We are looking forward to setting up business relationship with you and hope to provide you with the best service and solution. Let us make a better world for our industry!

Contact us

Tel: +86-755-8981 8866 Fax: +86-755-8427 6832 Email & Skype: info@chipsmall.com Web: www.chipsmall.com Address: A1208, Overseas Decoration Building, #122 Zhenhua RD., Futian, Shenzhen, China

MP4034 **Offline LED Driver**

The Future of Analog IC Technology

DESCRIPTION

The MP4034 is an offline regulator that provides accurate constant-current regulation. The LED driver circuit design is simplified by removing the opto-coupler and the secondary feedback components.

The MP4034 has an integrated 700V MOSFET. Its variable off-time control allows a flyback converter to operate in discontinuous conduction mode (DCM). The MP4034 also features complete protection functions such as VCC under-voltage lockout, over-voltage protection, over-temperature protection, and open-loop protection.

The MP4034's variable switching frequency provides natural spectrum shaping to smooth the EMI signature, which can reduce the EMI filter's size and cost.

FEATURES

- Primary-Side–Control without Opto-coupler or Secondary Feedback Circuit
- Precise Constant Current Regulation
- Integrated 700V MOSFET with Minimal External Components
- Variable Off-Time and Peak-Current Control
- 550µA High-Voltage Current Source
- Up to 7W Output Power
- Over-Voltage Protection
- Over-Temperature Protection
- Open-Loop Protection
- Natural Spectrum Shaping for Improved EMI Signature
- Low Cost and Simple External circuit
- SOIC8-7A Package

APPLICATIONS

Offline LED Driver

All MPS parts are lead-free and adhere to the RoHS directive. For MPS green status, please visit MPS website under Products, Quality Assurance page. "MPS" and "The Future of Analog IC Technology", are Registered Trademarks of Monolithic Power Systems, Inc.

MP4034 Rev. 1.03 www.MonolithicPower.com
1/23/2014 MPS Proprietary Information Patent Protected Unauthorized Photocopy and Duplication Prohibited MPS Proprietary Information. Patent Protected. Unauthorized Photocopy and Duplication Prohibited. © 2014 MPS. All Rights Reserved.

ORDERING INFORMATION

* For Tape & Reel, add suffix –Z (e.g. MP4034GS–Z);

PACKAGE REFERENCE

ABSOLUTE MAXIMUM RATINGS (1)

Recommended Operating Conditions **(3)**

Operating VCC range 6.6V to 28V Operating Junction Temp. (T_J) . -40°C to +125°C

Thermal Resistance **(4)** *θJA θJC* SOIC8-7A 76 45... °C/W

Notes:

- 1) Exceeding these ratings may damage the device.
- 2) The maximum allowable power dissipation is a function of the maximum junction temperature T_J (MAX), the junction-toambient thermal resistance θ_{JA} , and the ambient temperature T_A . The maximum allowable continuous power dissipation at any ambient temperature is calculated by P_D (MAX) = (T_J (MAX)-TA)/θJA. Exceeding the maximum allowable power dissipation will cause excessive die temperature, and the regulator will go into thermal shutdown. Internal thermal shutdown circuitry protects the device from permanent damage.
- 3) The device is not guaranteed to function outside of its operating conditions.
- 4) Measured on JESD51-7, 4-layer PCB.

ELECTRICAL CHARACTERISTICS

VCC = 15V, TA = 25°C, unless otherwise noted.

TYPICAL CHARACTERISTICS

mpc

TYPICAL CHARACTERISTICS *(continued)*

TYPICAL PERFORMANCE CHARACTERISTICS

Performance waveforms are tested on the evaluation board of the Design Example section. V_{IN} = 230VAC, V_{OUT} = 40V, I_{OUT} = 0.13A, L = 1.2mH, T_A = 25°C, unless otherwise noted.

MP4034 Rev. 1.03 www.MonolithicPower.com
1/23/2014 MPS Proprietary Information. Patent Protected. Unauthorized Photocopy and Duplication Prohibited. MPS Proprietary Information. Patent Protected. Unauthorized Photocopy and Duplication Prohibited. © 2014 MPS. All Rights Reserved.

TYPICAL PERFORMANCE CHARACTERISTICS *(continued)*

Performance waveforms are tested on the evaluation board of the Design Example section. V_{IN} = 230VAC, V_{OUT} = 40V, I_{OUT} = 0.13A, L = 1.2mH, T_A = 25°C, unless otherwise noted.

PIN FUNCTIONS

FUNCTIONAL BLOCK DIAGRAM

Figure 1: Functional Block Diagram

OPERATION

Figure 2: Simplified Flyback Converter

Startup

Initially, the IC is self-supplying through the internal high-voltage current source, which is drawn from the Drain pin. The internal highvoltage current source will turn off for better efficiency when V_{CC} reaches the V_{CC} ON threshold. Then the transformer's auxiliary winding takes over as the power source. When V_{CC} falls below the V_{CC} OFF threshold, the IC stops switching and the internal high-voltage current source turns on again. See Figure 3 for the start-up waveform.

Transformer Design

Figure 4: Isolated Flyback LED Driver

The MP4034 ensures that the circuit operates in discontinues conduction mode (DCM). When the IC internal MOSFET turns on, the current (i_P) flowing through transformer's primary-side winding (N_P) increases linearly until it reaches its peak current limit (I_{PK})

Figure 5: Current Waveform

Assume switching frequency is f_s , the power stored in the inductor is given by:

$$
P=\frac{1}{2}L_M\times I_{\text{PK}}^2\times f_{\text{S}}
$$

Then inductance of coupling inductor is then:

$$
L_M = \frac{2 \times P_o}{I_{PK}^2 \times f_s \times \eta}
$$

Where P_0 is output power and η is the estimated efficiency.

When MP4034's internal switch turns off, the freewheeling current (i_s) will flow through secondary-side diode and decrease linearly, as shown in Figure 5.

The relationship of peak current at ON period and OFF period is:

$$
I_{\mathsf{PK}_S}=\frac{N_\mathsf{P}}{N_\mathsf{S}}\!\times\!I_{\mathsf{PK}}
$$

Where $N_{\rm p}$ is the number of primary winding turns, and $N_{\rm s}$ is the number of secondary winding turns.

The MP4034 detects the secondary side diode duty cycle by sampling the auxiliary winding voltage and generates a ZCD signal as shown in Figure 6.

Figure 6: VFB and ZCD Waveforms

When the FB voltage is high—which means that the current is flowing through secondaryside diode—the ZCD signal goes high. Conversely, when the FB voltage is low—which means no current flows through the secondaryside diode—the ZCD signal goes low, meaning the secondary-side diode duty cycle (D_s) is:

$$
D_s = \frac{T_{s_on}}{T_{s_on} + T_{s_OFF}}
$$

Then the average output current is:

$$
I_{OUT} = \frac{1}{2} \times I_{PK_S} \times D_S
$$

=
$$
\frac{1}{2} \times \frac{N_p}{N_s} \times I_{PK} \times \frac{T_{s_ON}}{T_{s_ON} + T_{s_OFF}}
$$

The MP4034 keeps D_s at 0.4. Thus the output current is:

$$
I_{\text{OUT}} = \frac{1}{2} \times \frac{N_{\text{p}}}{N_{\text{S}}} \times I_{\text{PK}} \times D_{\text{S}} = \frac{1}{5} \times \frac{N_{\text{p}}}{N_{\text{S}}} \times I_{\text{PK}}
$$

This provides enough information to design the transformer turn ratio.

Leading-Edge Blanking

Turning the power switch on induces a spike on the sense resistor. To avoid falsely terminating the switching pulse, the MP4034 includes a 300ns leading-edge blanking period. During this blanking period, the current sense comparator is disabled and the gate driver can not switch off.

DCM Detection

The MP4034 is designed to operate in discontinuous conduction mode (DCM). To avoid operating in continuous conduction mode (CCM), the MP4034 detects the falling edge of the FB input voltage with each cycle. If the chip does not detect a 120mV falling edge, it will stop switching.

Over Voltage Protection

The MP4034 has two levels of over-voltage protection based on the FB voltage.

In normal operation, MP4034 samples the FB pin voltage 3.5μs after the primary switch turns off, as shown in Figure 6.

Figure 7: Auxiliary Voltage Waveform

The relationship of output voltage and V_{FB} is :

$$
V_{FB} = \frac{N_{P_A U}}{N_S} \times \frac{R_{\text{DOWN}}}{R_{\text{UP}} + R_{\text{DOWN}}} \times (V_{\text{O}} + V_{\text{D}})
$$

Where V_D is the secondary-diode forward-drop voltage.

When the MP4034 detects that the FB voltage equals 4.0V, the first level OVP triggers. The switching frequency drops to maintain the output voltage at a constant value. If V_{FB} voltage exceeds 6.35V for 3.5μs, it will shut down immediately and discharge the VCC

MP4034 Rev. 1.03 www.MonolithicPower.com
1/23/2014 MPS Proprietary Information. Patent Protected. Unauthorized Photocopy and Duplication Prohibited. MPS Proprietary Information. Patent Protected. Unauthorized Photocopy and Duplication Prohibited. © 2014 MPS. All Rights Reserved.

 \blacksquare

voltage. When V_{CC} drops to UVLO, the MP4034 will restart.

$$
\begin{array}{c}\n1 \\
2 \\
\hline\n\end{array}
$$
\n
$$
\begin{array}{c}\n1 \\
\hline\n\end{array}
$$
\n
$$
\begin{array}{c}\n1 \\
\hline\n\end{array}
$$
\n
$$
\begin{array}{c}\n1 \\
\hline\n\end{array}
$$
\n
$$
\begin{array}{c}\nN-1 \\
\hline\n\end{array}
$$
\n
$$
\begin{array}{c}\nN \\
\hline\n\end{array}
$$

Figure 8: LED String

Assume the forward voltage of one LED is V_F and the total number of LEDs on the string is N. So the output voltage can be calculated as $N \times V_F$. To ensure that OVP won't trigger during normal operation; the V_{FB} should not exceed V_{FBOVP1} (typical 4.0V). However, avoid a large output voltage when OVP occurs. So the voltage reflected on the FB pin should be:

$$
V_{_{FB}} = \frac{N_{_{P_AU}}}{N_{_{S}}} \times \frac{R_{\text{DOWN}}}{R_{\text{DOWN}} + R_{_{UP}}} \times (N \times V_{_{F}} + V_{_{D}}) = 0.85 V_{_{FBOVP1}}
$$

Open-Circuit Protection (OCkP)

The MP4034 has open-circuit protection (OCkP). If the $-0.15V$ falling edge of V_{FB} can not be monitored—which means the feedback loop is open—the MP4034 immediately shuts off the driving signals and enters hiccup mode. The MP4034 resumes normal operation when the fault has been removed.

Thermal Shutdown (TSD)

When the temperature of the IC exceeds 150°C, the over-temperature protection is enacted and the IC enters auto-recovery mode. When the temperature falls below 120°C, the IC resumes working.

APPLICATION INFORMATION

COMPONENT SELECTION

Input Filter

Input filter produces a DC source through the rectifier from the AC input power Figure 9 shows the input filter and Figure 10 shows the typical DC bus voltage waveform.

Figure 10: DC Input-Voltage Waveform

Bulk capacitors C1 and C2 filter the rectified AC. Inductor L forms a π filter with C1 and C2 to restrain the differential-mode EMI noise. The resistor (R) in parallel with the inductor (L) restrains the mid-frequency-band EMI noise. Normally, R is selected between 1kΩ and 10kΩ.

The DC input capacitors, C1 and C2, are usually 2µF/W to 3µF/W for the universal input condition. For a 230VAC single-range application, the capacitor can be half that value. Normally, the minimum DC voltage should not be too low to ensure the converter can supply the maximum power to the load which can be express as follows:

$$
V_{DC(min)} \geq \frac{N_\text{p}}{N_\text{s}}\cdot\left(N\cdot V_\text{F} + V_\text{D}\right)\cdot\frac{D_\text{s}}{1-D_\text{s}}
$$

If the $V_{DC(min)}$ can not satisfy this express, increase the value of the input capacitors to increase the $V_{DC(min)}$.

Output Diode

Use a Schottky diode because of its fast switching speed and low forward voltage drop for better efficiency.

If a lower average efficiency (3%-4%) is acceptable, replace the output diode with a PNjunction diode or other non-Schottky diode to lower costs.

Leakage Inductance

The transformer leakage inductance will decrease the system efficiency and affect the output current constant precision. The transformer structure should be optimized to improve the primary side and secondary side coupling and minimize the transformer leakage inductance of transformer. Aim for a leakage inductance that is less than 5% inductance.

RCD Snubber

The transformer leakage inductance causes the MOSFET drain voltage spike and the excessive ringing on the drain voltage waveform.

The RCD snubber circuit can limit this Drain voltage spike. Figure 11 shows the RCD snubber circuit.

Figure 11: RCD Snubber

MP4034 Rev. 1.03 www.MonolithicPower.com
13/2014 MPS Proprietary Information. Patent Protected. Unauthorized Photocopy and Duplication Prohibited. MPS Proprietary Information. Patent Protected. Unauthorized Photocopy and Duplication Prohibited. © 2014 MPS. All Rights Reserved.

Select R_{SN} and C_{SN} for an acceptable voltage spike and better system operation.

The power dissipated in the snubber circuit is approximately:

$$
P_{\text{SN}} = \frac{1}{2} \cdot L_{\text{K}} \cdot I_{\text{PK}}^2 \cdot \frac{V_{\text{SN}}}{V_{\text{SN}} - N_{\text{PS}} \times V_{\text{O}}} \times f_{\text{S}}
$$

Where:

- L_K is the leakage inductance,
- V_{SN} is the clamp voltage,
- N_{PS} is the turn ratio of primary and secondary side.

The power consumed in the snubber resistor (R_{SN}) , the resistor (R_{SN}) is:

$$
R_{\text{SN}} = \frac{V_{\text{SN}}^2}{P_{\text{SN}}}
$$

The maximum ripple of the snubber capacitor voltage is:

$$
\Delta V_{\rm SN} = \frac{V_{\rm SN}}{C_{\rm SN} \cdot R_{\rm SN} \cdot f_{\rm S}}
$$

Generally, a 15% ripple is reasonable. Use the previous equation to approximate C_{SN} .

The damping resistor (R) in series with the RCD has a relatively large value to prevent any excessive ringing voltage that can affect the EMI. Use a damping resistor of about 200Ω to 500Ω to limit the drain voltage ringing.

Resistor Divider

For better application performance, use a resistor divider with values in the range of 10kΩ to 100kΩ to limit noise from adjacent components on the FB pin. Connect a resistor with a value ranging from 1kΩ to 2kΩ from the FB pin to the resistor divider to limit substrate injection current effects, as shown in Figure 12.

Figure 12: FB Pin in Series with ON Resistor

Dummy Load

A dummy load is required in open-output applications for good over-voltage protection. Use a dummy load of ~10mW for good load regulation.

Maximum Switching Frequency

Because of the parameter tolerance of the sampling detecting time and inductance tolerances, select a secondary-side-diode conduction time that exceeds 5.4µs as follows.

$$
T_{s_ON} = I_{PK} \cdot \frac{N_s \cdot L_M}{N_P \cdot (V_O + V_D)} > 5.4 \mu s
$$

For high or low temperature operation, select a maximum switching frequency below 75kHz.

PCB Layout Guide

PCB layout is very important to achieve reliable operation, and good EMI and thermal performance. The use design guide as follows to help optimize performance.

1. Minimize the loop area formed by the input capacitor, the MP4034 drain-source, and the primary winding to reduce EMI noise.

2. The copper area connected to source pins acts as a heat sink. Provide a large copper area to improve the thermal performance.

3. Minimize the clamp circuit loop to reduce EMI.

4. Minimize the secondary loop area of the output diode and output filter to reduce the EMI noise. In addition, provide a sufficient copper area at the anode and cathode terminal of the output diode for heat dissipation.

5. Place the AC input away from the switching nodes to minimize the noise coupling that may bypass the input filter.

6. Place the bypass capacitor as close as possible to the IC and source.

7. Place the feedback resistors at the FB pin and minimize the feedback sampling loop area to minimize noise coupling.

8. Use a single point connection at the negative terminal of the input filter capacitor for the MP4034 source pin and bias winding return.

Figure 13 shows a layout example.

Top Layer

Bottom Layer

Figure 13: PCB Layout Design Example

Below are design examples following the application guidelines for the given specifications:

Figure 14 and Figure 15 show the detailed isolated application, while Figure 16 and Figure 17 show the detailed non-isolated application. These examples were used in the Typical Performance Characteristics section. For more applications, please refer to the related evaluation board datasheets.

TYPICAL APPLICATION CIRCUITS

Universal Input, Driving 14 LEDs in Series, 130mA LED Current, 6W Isolation Flyback Converter

Figure 15: Typical Application Example Universal Input, Driving 3 LEDs in Series, 350mA LED Current, 3.5W Isolation Flyback Converter

Figure 16: Typical Application Example Universal Input, Driving 14 LEDs in Series, 150mA LED Current, 6W Non-isolated Buck-Boost Converter

Figure 17: Typical Application Example Universal Input, Driving 3 LEDs in Series, 350mA LED Current, 3.5W Non-isolated Buck-Boost Converter

FLOW CHART

PACKAGE INFORMATION

NOTICE: The information in this document is subject to change without notice. Users should warrant and guarantee that third party Intellectual Property rights are not infringed upon when integrating MPS products into any application. MPS will not assume any legal responsibility for any said applications.