



Chipsmall Limited consists of a professional team with an average of over 10 year of expertise in the distribution of electronic components. Based in Hongkong, we have already established firm and mutual-benefit business relationships with customers from,Europe,America and south Asia,supplying obsolete and hard-to-find components to meet their specific needs.

With the principle of “Quality Parts,Customers Priority,Honest Operation,and Considerate Service”,our business mainly focus on the distribution of electronic components. Line cards we deal with include Microchip,ALPS,ROHM,Xilinx,Pulse,ON,Everlight and Freescale. Main products comprise IC,Modules,Potentiometer,IC Socket,Relay,Connector.Our parts cover such applications as commercial,industrial, and automotives areas.

We are looking forward to setting up business relationship with you and hope to provide you with the best service and solution. Let us make a better world for our industry!



## Contact us

Tel: +86-755-8981 8866 Fax: +86-755-8427 6832

Email & Skype: info@chipsmall.com Web: www.chipsmall.com

Address: A1208, Overseas Decoration Building, #122 Zhenhua RD., Futian, Shenzhen, China






**ON Semiconductor®**

# Test Procedure for the NCP1565 3.3-V/20-A Dc-dc Converter



# Board Electrical Schematic

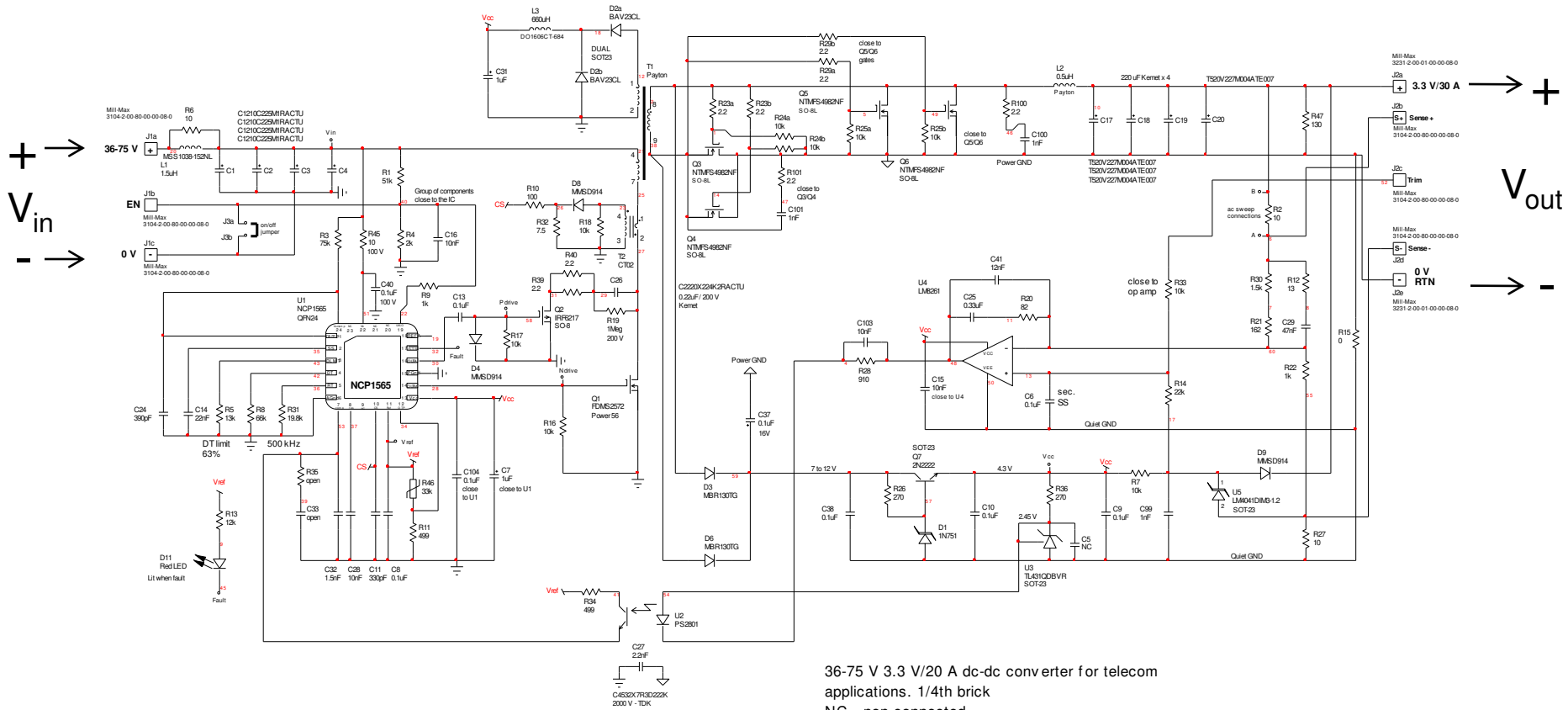

36-75 V 3.3 V/20 A dc-dc converter for telecom applications. 1/4th brick  
 NC - non connected


ON Semiconductor  
 Christophe Basso - February 17th 2014.  
 Rev 1c.  
 PCB rev 1

Dc input voltage  
 36 – 72 V

3.3 V/20 A  
 Output voltage



# Board Picture

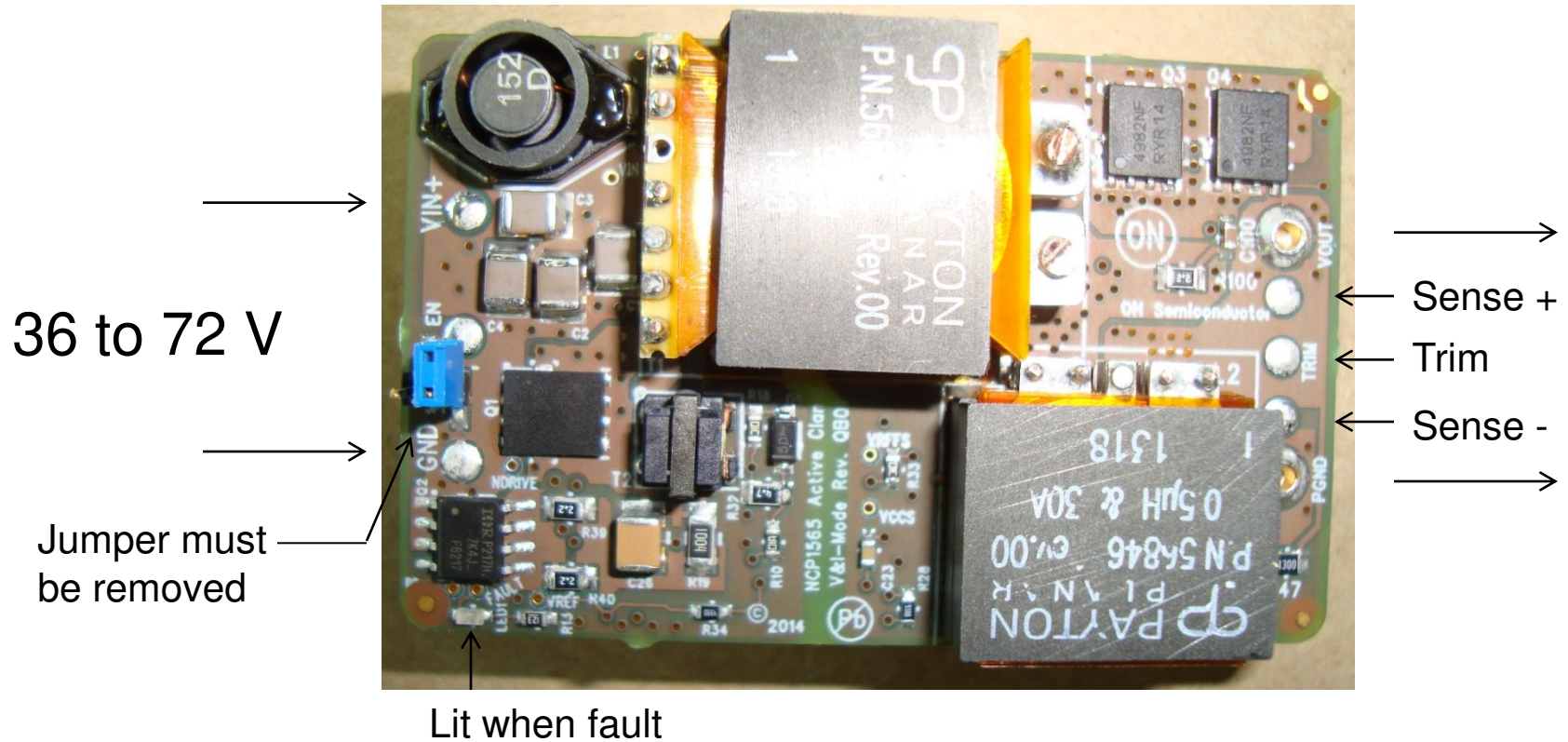

Input voltage from 36 V to 72 V  
dc. Nominal input is 48 V

Output voltage is 3.3 V  
nominal current is 20 A

# Needed Equipment

The needed equipments are the following:

- ❑ a dc voltage source, delivering up to 80 V dc and up to 3 A
- ❑ a dc load absorbing up to 100 W,  $V_{in,max} < 20 \text{ V}$ ,  $I_{out,max} < 40 \text{ A}$
- ❑ either the above load can display dc V and dc A or separated V and A-meters are necessary
- ❑ An oscilloscope with single shot capability
- *Kelvin sensing is necessary to connect the load to the board. If no precautions are taken, it is likely that the voltage drop at the load cables ends induces a reading error*




# Basic Test Setup


source



load

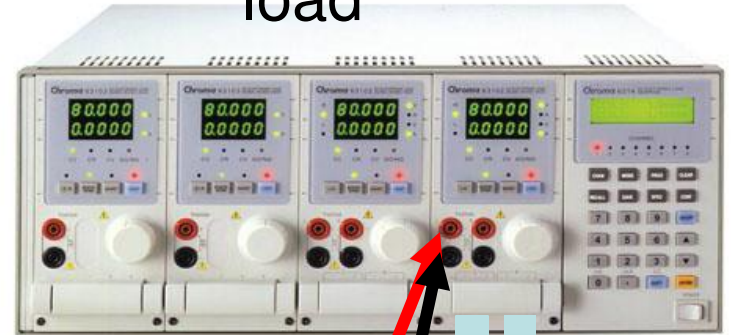


Jumper is removed

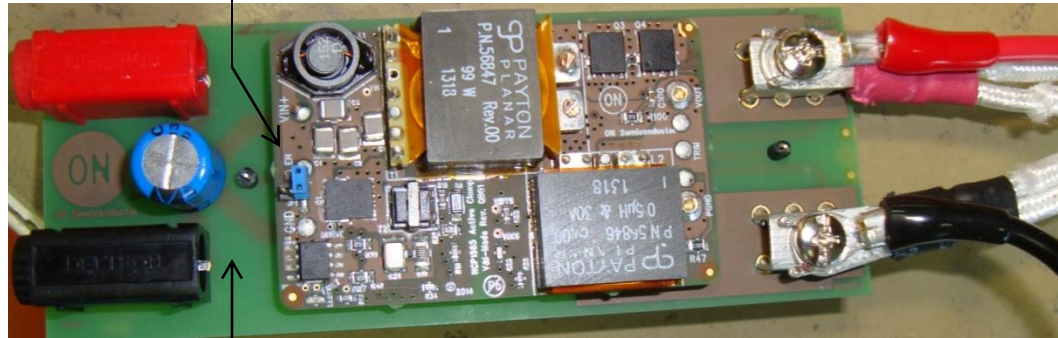

Socket in which the dc-dc is firmly plugged

Kelvin sense


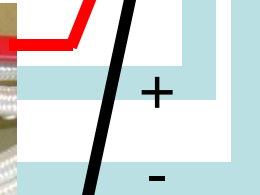


# Test n°1

Source = 36 V




Load = 20 A

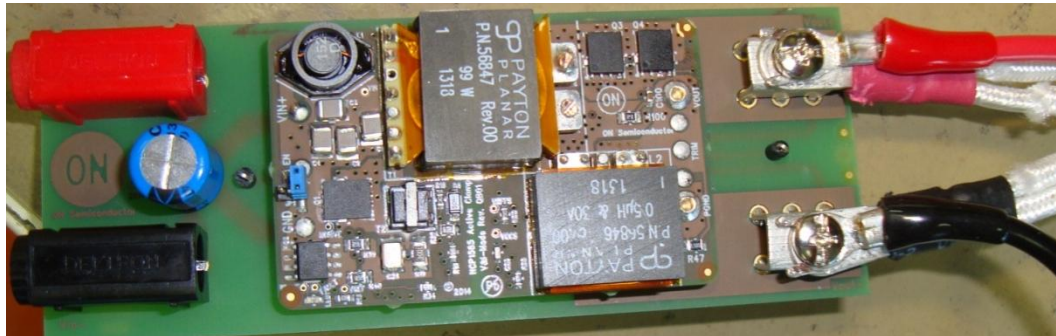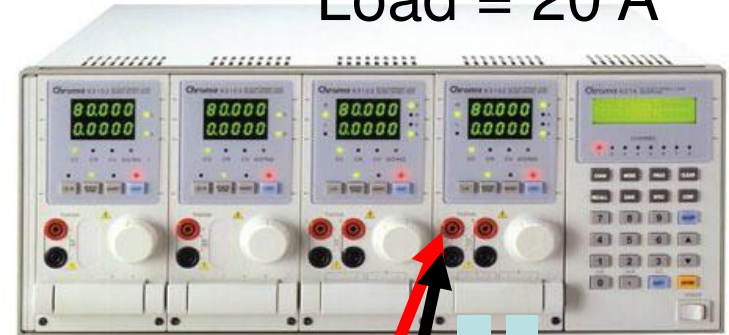


- Start the power supply while the load current is 20 A
- Monitor the output voltage on a scope
- Verify the voltage is monotonically rising



# Test n°1

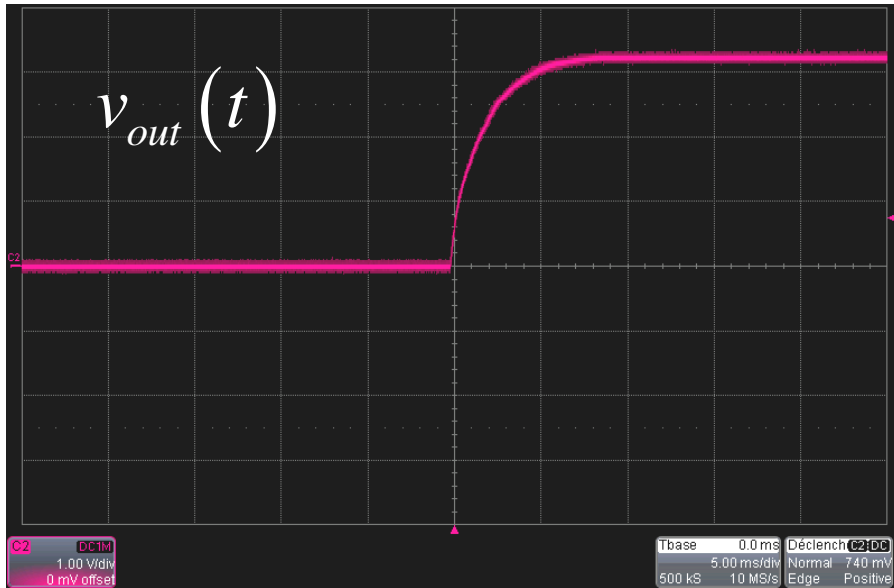

Ok

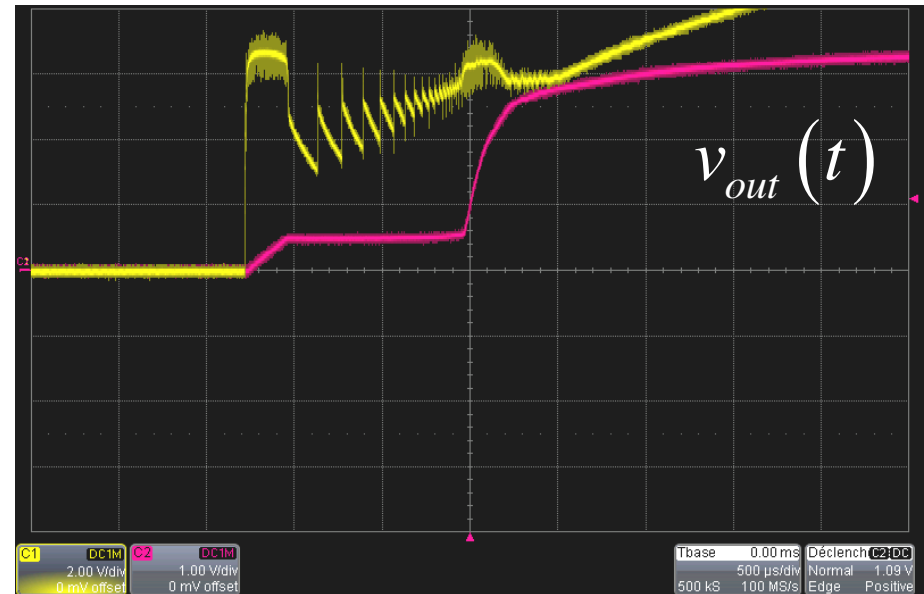

Bad

- It is important to verify the absence of double slope
- Repeat the test for  $V_{in} = 48\text{ V}$  and  $72\text{ V}$
- Change load to  $0\text{ A}$ , repeat tests. Wait  $10\text{ s}$  between re-starts.




# Test n°2

source



load

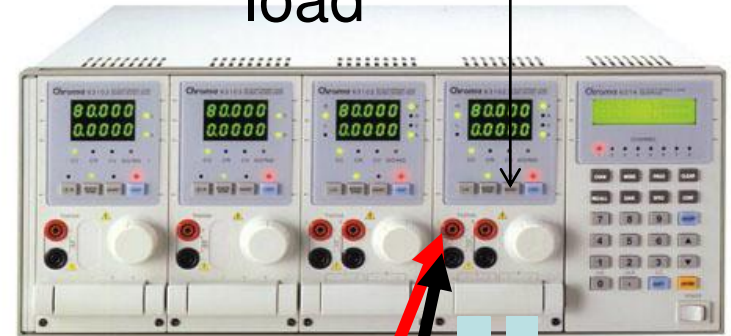

Jumper is removed





- Press short circuit at  $V_{in} = 36\text{ V}$ . Led blinks, board ticks.
- Repeat test for  $V_{in} = 48\text{ V}$  and  $72\text{ V}$
- Release short and make sure output resumes at  $3.3\text{ V}$ .

# Test n°3

source



load

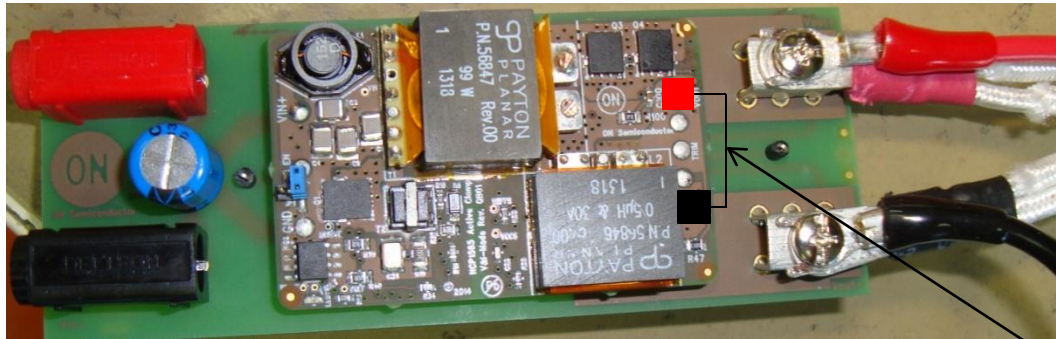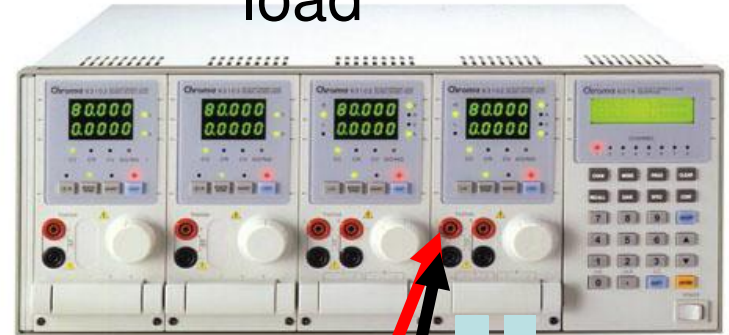


Probe here




No pigtail!

- Program load to dynamic current mode
- $I_{out}$  from 20 A to 15 A, slope 1 A/ $\mu$ s
- 1 ms interval, observe  $V_{out}$  on scope in ac, 20 mV/div

# Test n°3

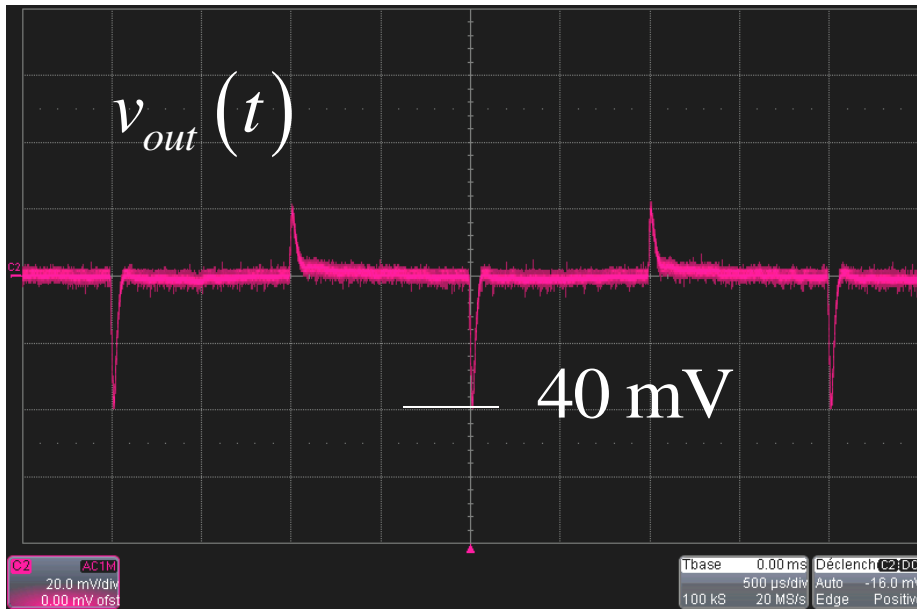

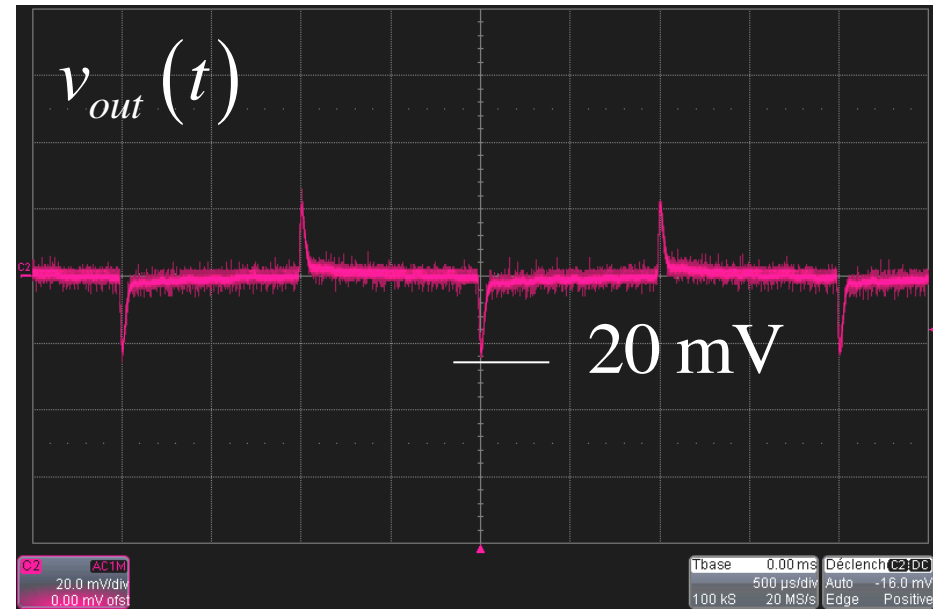$V_{in} = 36 \text{ V}$   $I_{out} = 15 \text{ to } 20 \text{ A}$ ,  $1 \text{ A}/\mu\text{s}$



$V_{in} = 48 \text{ V}$   $I_{out} = 15 \text{ to } 20 \text{ A}$ ,  $1 \text{ A}/\mu\text{s}$



- Run the test from  $V_{in} = 36 \text{ V}$  (worst case) to  $V_{in} = 72 \text{ V}$ .
- Spec is to have an under/over shoot less than 60 mV

# Test n°4

source



load

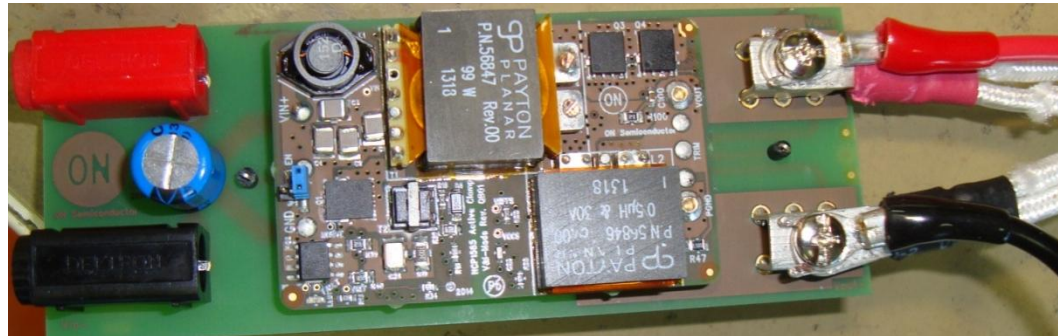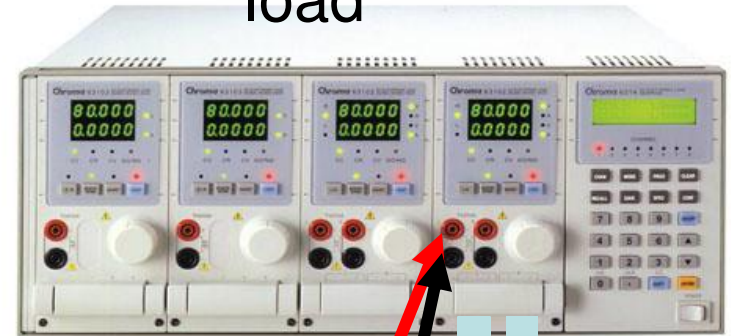

- Leave the board for 5 mn at  $V_{in} = 36 \text{ V}/20 \text{ A}$ .
- Check no thermal disjonction occurs.
- Board is declared sound.

